

# *Lecture 3. Opamp Design Basics*

**Prof. Guoyong Shi**

**[shiguoyong@sjtu.edu.cn](mailto:shiguoyong@sjtu.edu.cn)**

**Dept of Micro/Nano-electronics**

**Shanghai Jiao Tong University**

**Fall 2015**

# Contents

- **Opamp specs**
- **Building blocks**
- **Circuit-level design of LM741**
- **Terminologies**
  - **Input Common Mode Range (ICMR)**
  - **Offset voltage/current,**
  - **Output impedance, slew rate, noise**
  - **PMRR, CMRR,**
  - **Gain/phase margin, etc.**
- **Simple design tips**

# *Opamp Design Basics*


# Opamp Design Metrics

- **Design parameters**
  - Input bias current
  - Input offset voltage
  - Input offset current
  - Output impedance
  - Slew rate (SR)
  - Noise
  - Distortion
  - CMRR
  - PSRR
  - Gain and phase margins
  - Power & speed


- It's not possible to achieve all these goals by one single opamp stage.
- That's way we need to learn **multi-stage opamp design.**
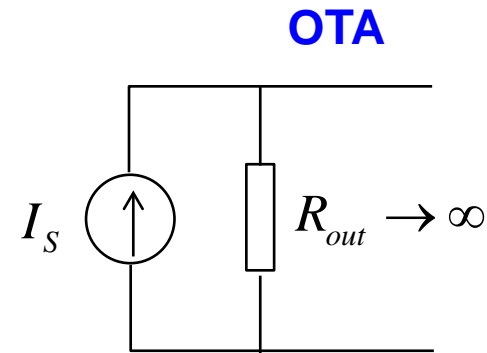
# Opamp Basics


- **Opamp basics**
  - **Biasing circuit**
  - **Differential input stage**
  - **Voltage gain stage**
  - **Output stage**




 
- **Feature of opamps**
  - **Very high input impedance (drawing no current)**
  - **Very low output impedance (as voltage source)**
  - **Very high open-loop gain**
  - **Differential input stage**
  - **Feedback for stability**




# Typical Opamp Building Blocks

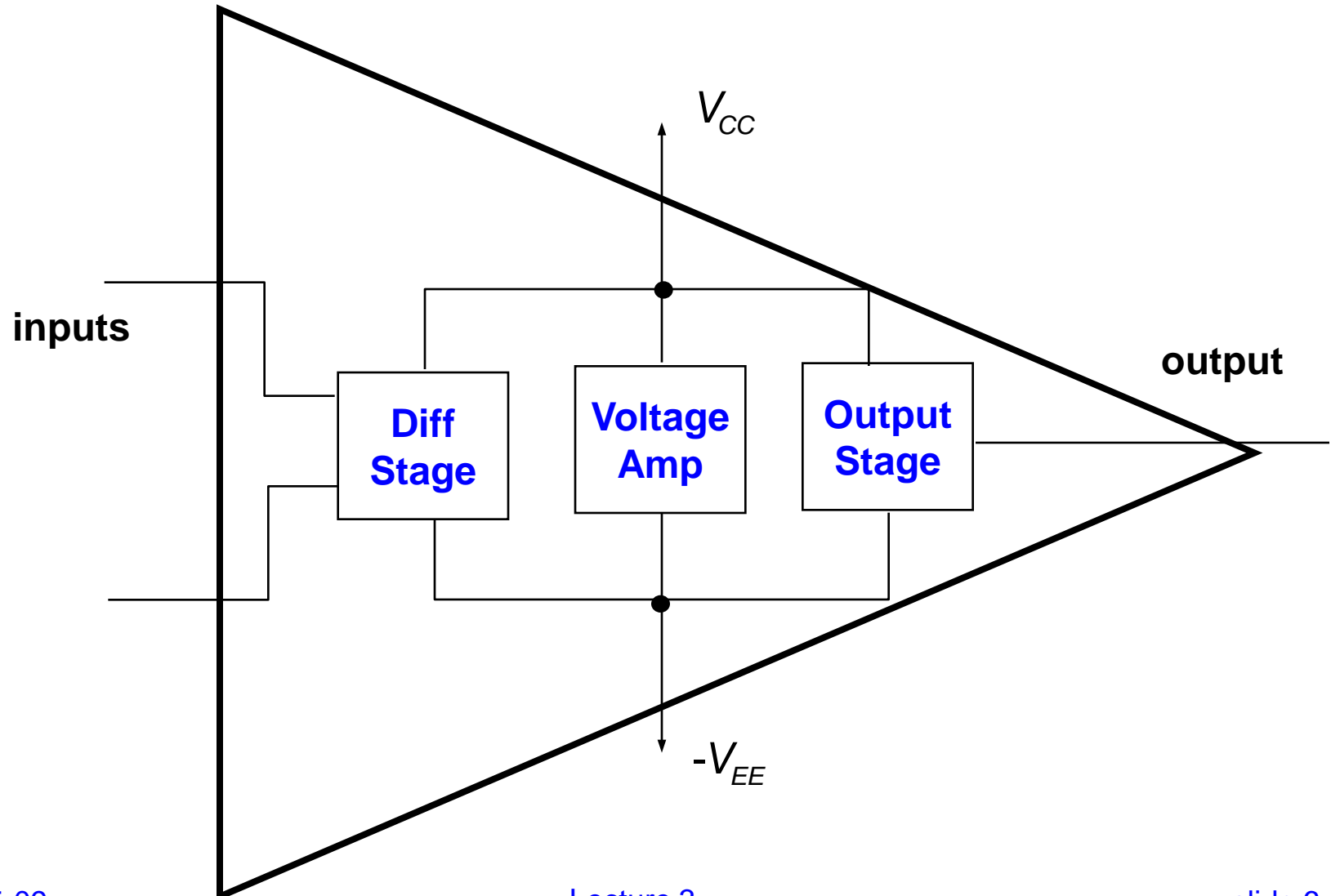

# Opamp as a VCVS

  


**VCVS model**

 

**High input impedance**

**Ideally zero output impedance**

 

**Nullator**

**Norator**

$$v_{k,m} = \textit{arbitrary}$$

$$i_{k,m} = \textit{arbitrary}$$

**Ideally it can be modeled by a nullor (a pair of nullator & norator)**

# *Opamp Applications*

- **Opamp has many applications**
  - **Comparators (infinite gain, open-loop)**
  - **Oscillators (open-loop opamp)**
  - **Filters (Switched-capacitor circuits)**
  - **Sensors**
  - **Sample and Hold (S&H)**
  - **Instrumentation amplifier**
  - **DC-DC converter**




# *What is Biasing ?*

- **Transistor Biasing** is the process of setting a transistor's DC operating voltage/current conditions properly so that any AC input signal can be amplified efficiently.
- If a transistor is properly biased to have a suitable operating point (OP), it can operate like a **linear amplifier** nearby the OP.

# *Opamp Structure*

**Using bipolar LM741 as an example**


# Opamp LM741 Circuit

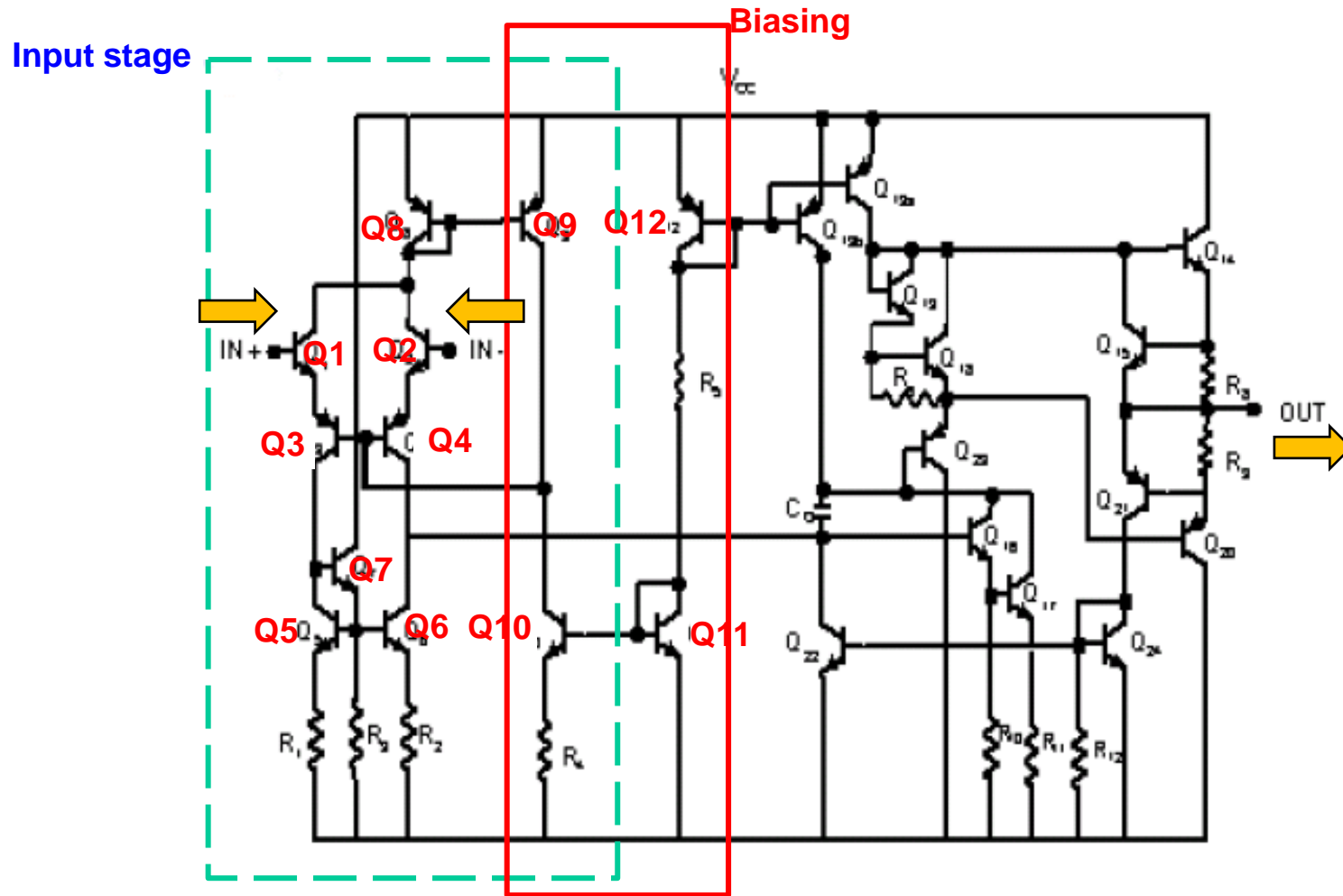

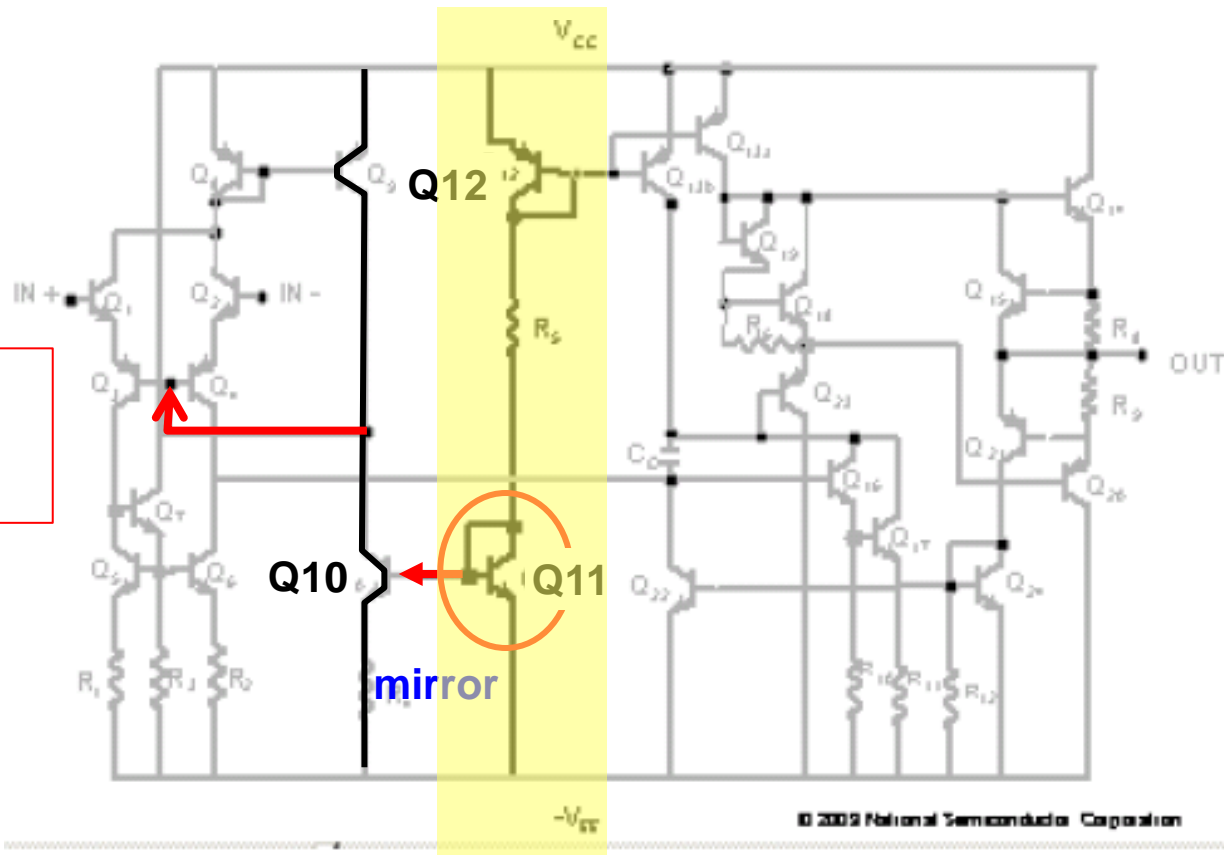
# Biasing Circuit

The branch of “Q12, R5, Q11” provides the **biasing current**.

The current is delivered to the input stage by the mirror pair (Q10, Q11).




# Differential Amplifier (Input)

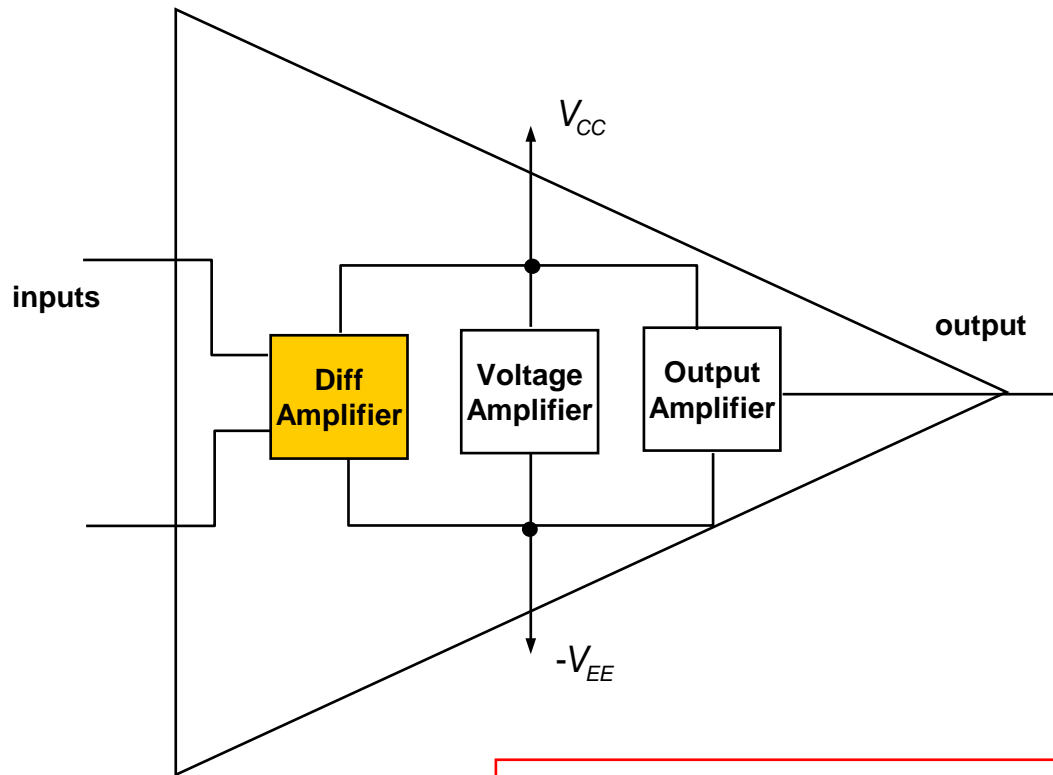

- Provides differential input and **dc gain**
- With **high input impedance**
- Drawing **negligible input current**

# Differential Input Stage

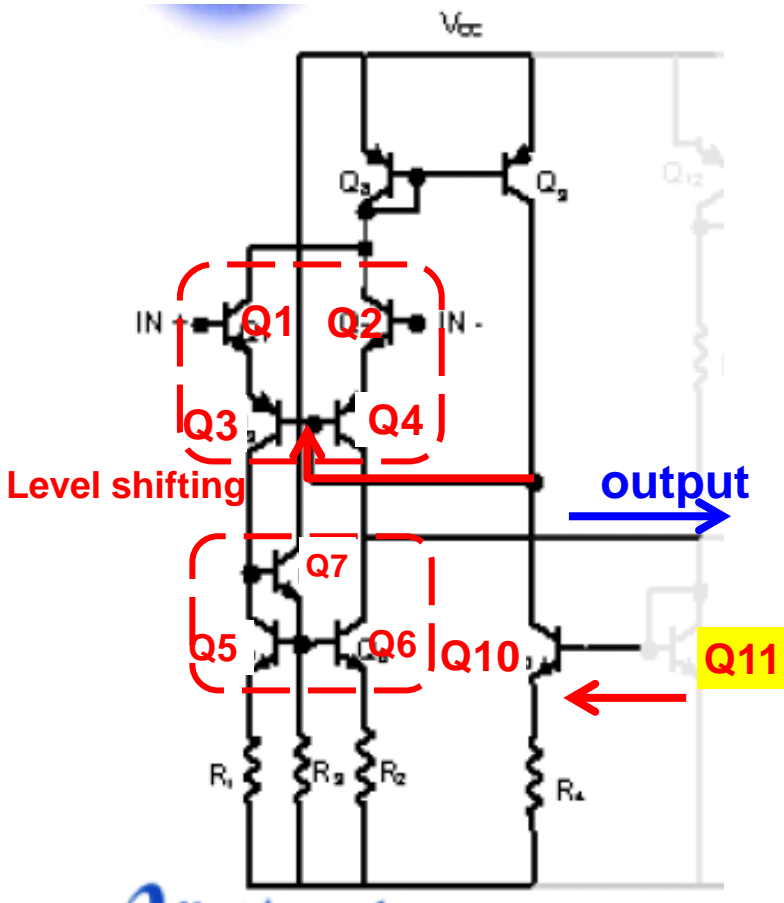


(Q1, Q2) connected with (Q3, Q4) as **emitter followers** – giving **high input impedance**.

(Q3, Q4) provide **dc level shifting**.

(Q5, Q6, Q7) load the input stage and converts **differential signal to single-ended signal**

# High-Gain Voltage Amplifier (Middle)

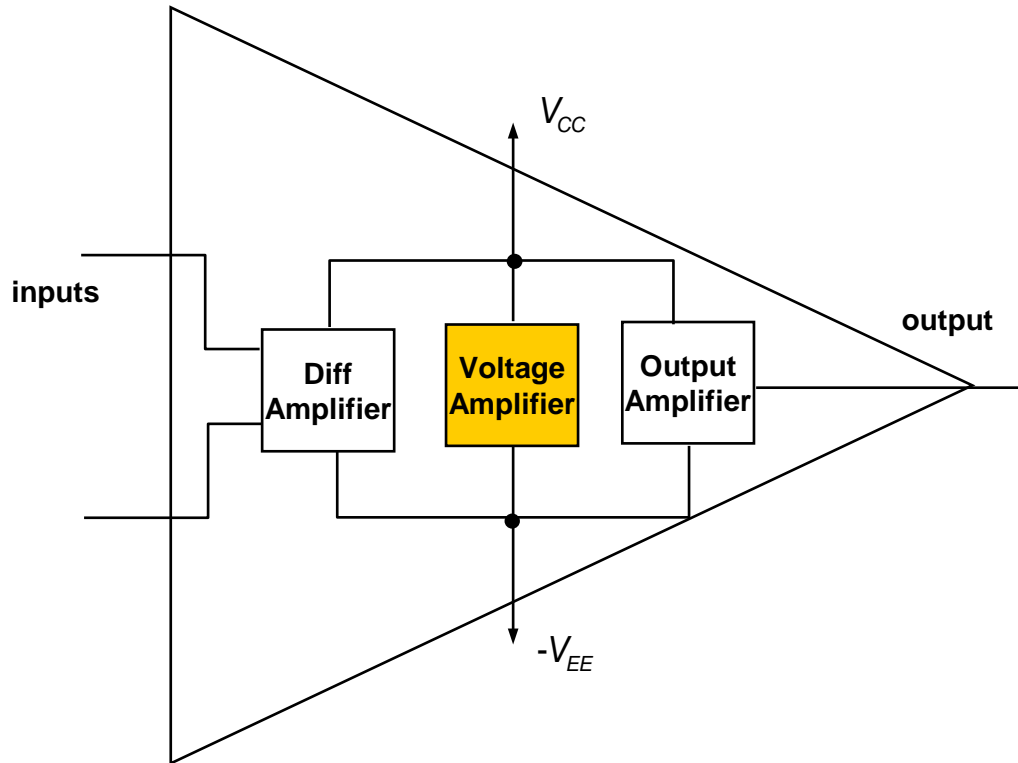

- Provides voltage “gain”
- Conveying it to the output stage

# Voltage Gain Stage (Middle)

## Q16-Q17 emitter follower


giving **high input resistance** to this stage;

Providing **high output resistance**

signal coming from the 1<sup>st</sup> stage




**C<sub>c</sub> Miller compensation**

 



# Low Impedance Output Stage

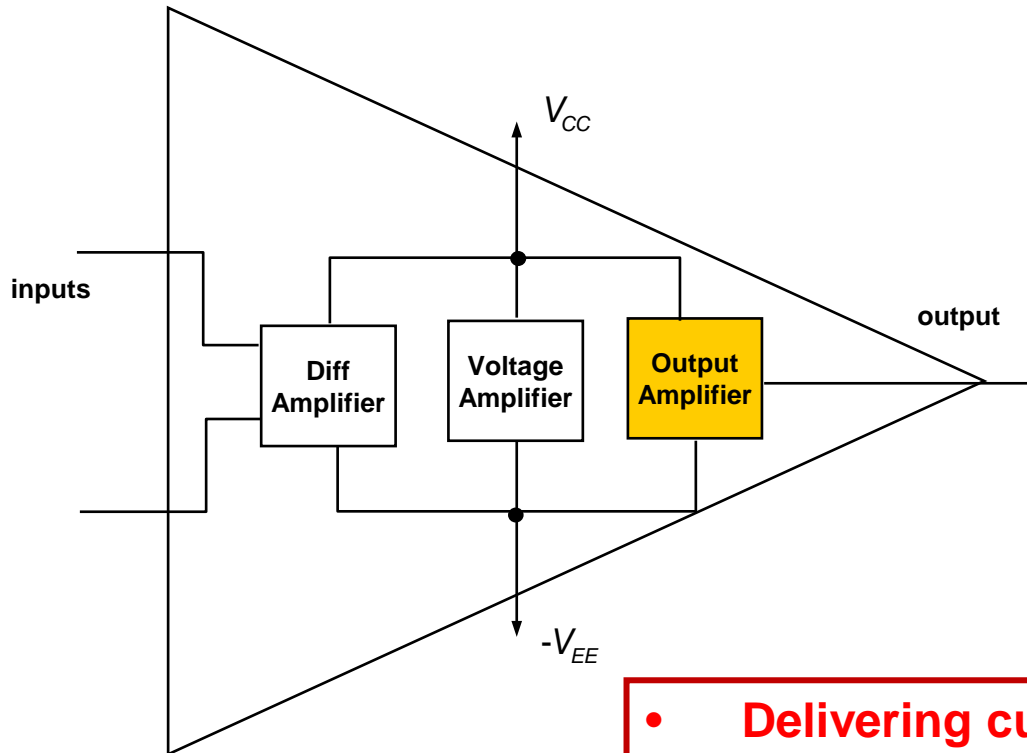

- Delivering current to the load;
- Very low output impedance (minimize self-loading)
- Providing short circuit protection

# Class AB Output Stage

**(Q14, Q20)** form complementary output stage (class AB, better power efficiency);


supplying fairly large (positive/negative) current to load;

Negligible temperature effect.

Low output impedance.

**(Q18, Q19)** bias the output transistor in linear region

 **(Q15, Q21)** for short circuit protection by shunting overflow current




# Summary

---

- **CMOS opamp circuit can be analyzed analogously**
- **Stage-based design helps intuition**
- **An opamp has a main signal path and some feedback compensations**
- **Detailed analysis has to go small-signal**

# Differential Input

 

Input signals are 180 degree out of phase.


Output is in-phase with the non-inverting input.

In general, op-amps can be set up in **three different input modes**:

- (1) differential input mode,
- (2) inverting input mode,
- (3) non-inverting input mode.


When the input signals are **in-phase**, there should be no output. Such input signal is called **the common-mode signal** (this property is used in testing opamp)

# Opamp working @ Inverting Input Mode

 

- The non-inverting input is grounded or connected to a fixed supply.
- The output is **180 degree out of phase** with the input.

# Working @ Non-inverting Input Mode

 


- The inverting input is grounded.
- The output is **in-phase** with the input.

# Open-loop vs Closed-loop

- **Open-loop**
  - Very high gain
  - Noise and other “unwanted” signals are amplified by the same gain factor (poor stability)
  - Open-loop used in comparators and oscillators (intentionally making use of instability)
- **Closed-loop**
  - Reduces the gain of amplifier
  - But improves the stability
  - Most applications use closed-loop opamps

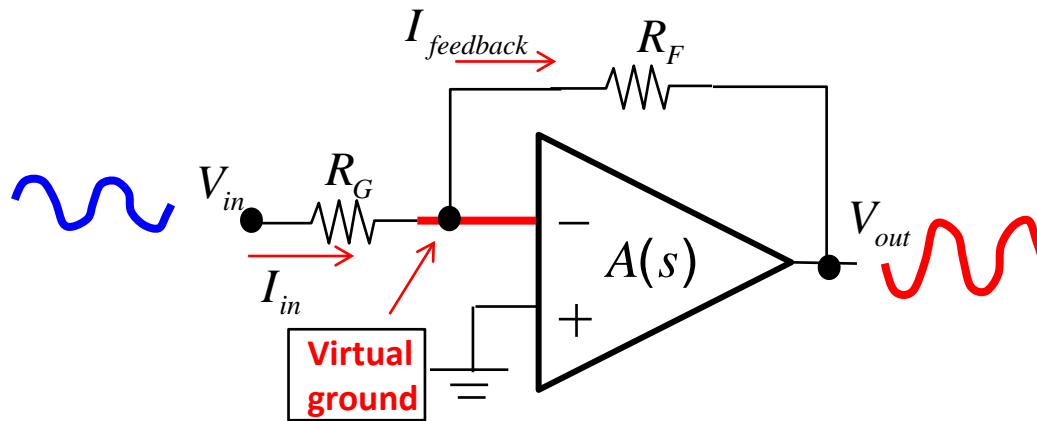
# Closed-Loop Configurations

**Inverting** closed-loop  
(out of phase)



$$\frac{V_{out}}{V_{in}} = -\frac{R_F}{R_G}$$

 **Non-Inverting** closed-loop  
(in-phase)



$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_F}{R_G}$$





# *Detailed Definitions of Opamp Metrics*

---

- **Input offset voltage, Input bias current, Input offset current**
- **Output impedance**
- **Internal/external noise**
- **CMRR / PSRR**

  
# Input Offset Voltage

- Ideally, when the two inputs are equal ( $\Delta = 0$ ), the output should be at the **mid-supply**.
- In reality (due to dc offset of the circuit) we have to apply a small input dc voltage difference to make the output settle at the mid-supply.
- Such a **dc input voltage difference** is called the “**Input Offset Voltage ( $V_{OS}$ )**”.


 
# Input Bias Current


- Ideally should be zero, but practically not.
- **Positive input bias current:**
  - Small current seen on the non-inverting input
- **Negative input bias current:**
  - Small current seen on the inverting input
- **Input bias current ( $I_{BIAS}$ )**
  - Average of the two currents at the inputs.



# Input Offset Current


- Ideally input currents should be equal to obtain zero output voltage.
- In reality, one has to set unequal input currents to make the output voltage zero.
- **Input offset current ( $I_{OS}$ ):** is the difference of the two input currents to achieve the zero output voltage.

$$I_{OS} = I_{in+} - I_{in-}$$

 
 
# Output Impedance ( $Z_{OUT}$ )


- Ideally should be **zero**.
- It is usually “assumed” to be zero
  - This way an op-amp behaves like **an ideal voltage source**.
  - It is capable of driving a wide range of loads.


 
# Internal Noise

- Caused by internal components, bias current, and drift.
- Internal noise can be converted to “input referred noise”.
- Noise or “unwanted” signal is amplified along with the “wanted” signal.
- Noise is amplified from the **non-inverting input** with a noise gain:
- **Noise gain =  $1 + (R_F/R_G)$**

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_F}{R_G}$$




# External Noise


- **Caused by external electrical devices and components**
  - **Power supply noise**
  - **Feedback resistor noise**
  - **Package noise**
- **These noises can be suppressed by proper circuit construction technique**
  - Adequate shielding
  - **Reduce resistor values** when possible
 
# Common Mode Rejection

- When **both inputs have the “common” voltage**, such a signal is called a **common mode signal**.
- Output should be **ideally zero** for the common mode input, i.e., **common-mode rejection**.
- A basic feature of differential amplifiers



**Common mode gain ( $A_{CM}$ )**

 

**Differential gain ( $A_d$ )**



# CMRR

- **Common Mode Rejection Ratio (CMRR)**
- Ratio of differential gain ( $A_d$ ) to common-mode gain ( $A_{CM}$ ), expressed in dB.
- **Typically decreases with frequency.**

$$CMRR = 20 \log \left| \frac{A_d}{A_{CM}} \right| = 20 \log \left| \frac{\Delta V_{OS}}{\Delta V_{CM}} \right|$$

$A_d$  : Differential gain

$A_{CM}$  : Common mode gain


$V_{OS}$  : Offset voltage (output)

$V_{CM}$  : Common mode voltage (output)

**There is another simulation-based measurement method for CMRR (see another lecture)**


 
# Power Supply Rejection Ratio (PSRR)

- Ratio of differential gain to small-signal gain of the **power supply**
- Or ratio of change in offset error to change in power supply voltage



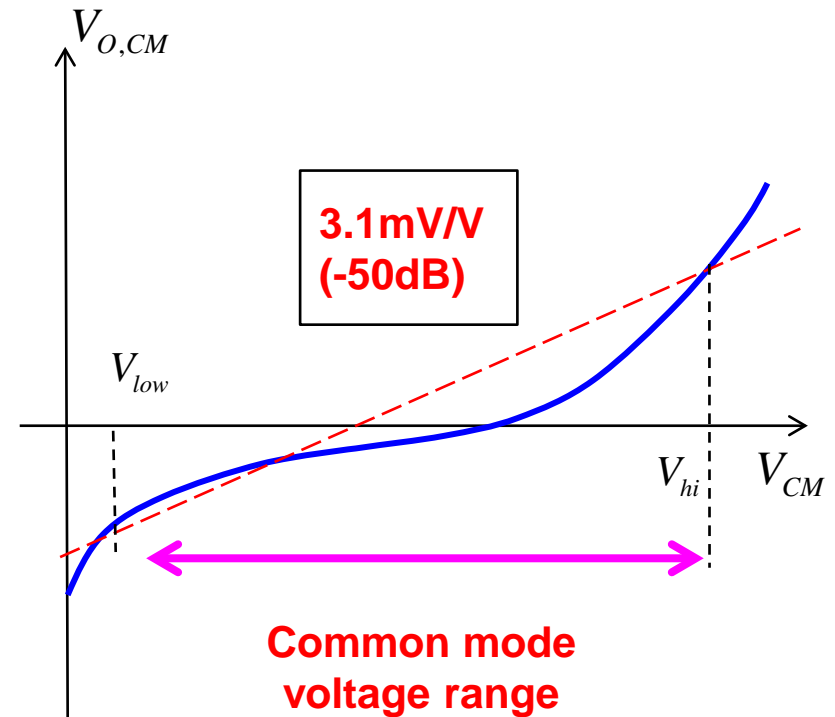 
# Common Mode Voltage Range

Range of the common input voltage  $V_{CM}$ ,  $[V_{low}, V_{hi}]$ , within which the differential pair behaves as a linear amplifier.



# Input Common Mode Range

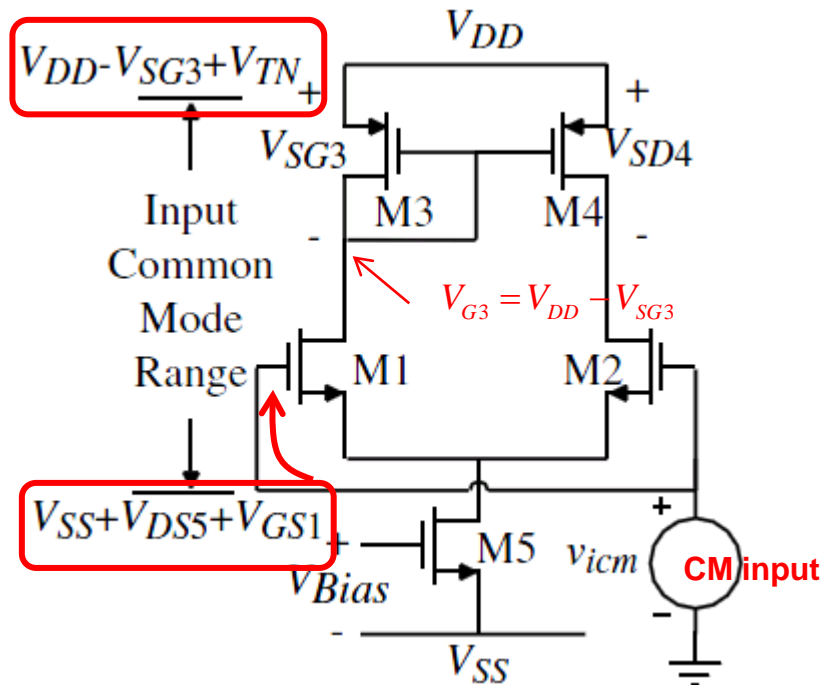

ICM Range is the largest voltage interval that the CM input can swing.

Max of  $V_{cm,in}$ :

$$V_{DD} - V_{SG3} + V_{TN}$$

Min of  $V_{cm,in}$ :

$$V_{SS} + V_{DS5} + V_{GS1}$$

Diff amp. with a current mirror load

$$V_{DS1} \geq V_{GS1} - V_{TN} \quad \Rightarrow \quad V_{G1,max} = V_{D1} + V_{TN} = V_{G3} + V_{TN}$$


Courtesy Paul Allen's lecture

# Input Common Mode Range

$$V_{SD3} = V_{SG3} - |V_{TP}| \leq V_{SG3} \quad \text{higher} \quad \boxed{V_{DD} - V_{SD3} + V_{TN}}$$

$$\Rightarrow V_{DD} - \boxed{V_{SG3}} + V_{TN} \leq V_{DD} - \boxed{V_{SD3}} + V_{TN}$$
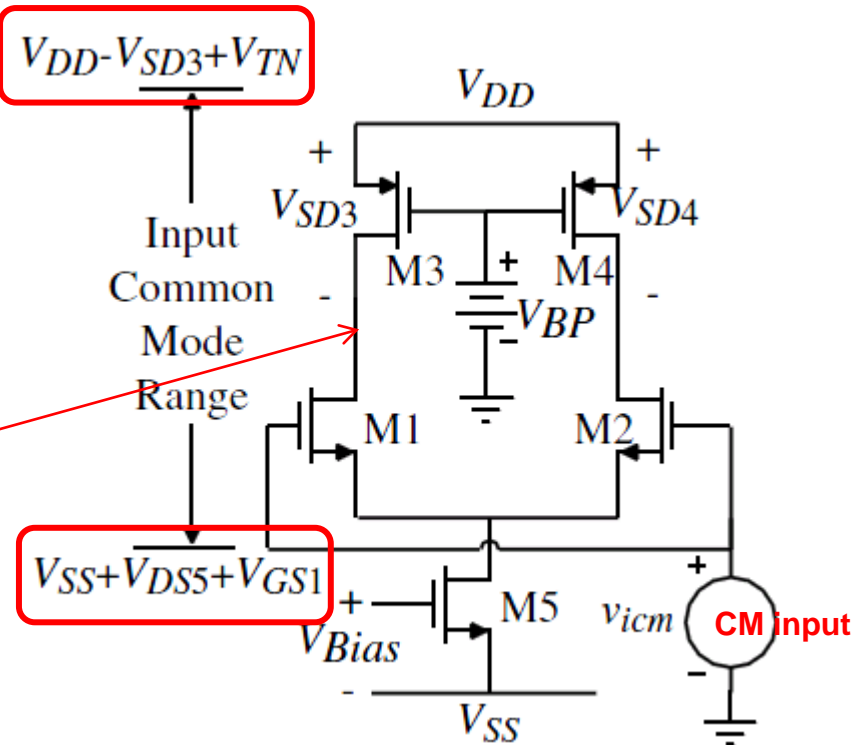
$$V_{D1} = \boxed{V_{G3}} = V_{DD} - V_{SD3}$$




Diff amp. with a current source load


Using current source load improves the ICMR.

$$V_{DS1} \geq V_{GS1} - V_{TN} \quad \Rightarrow \quad V_{G1,\max} = V_{D1} + V_{TN} = \boxed{V_{G3}} + V_{TN}$$

# ICM Range (Comparison)

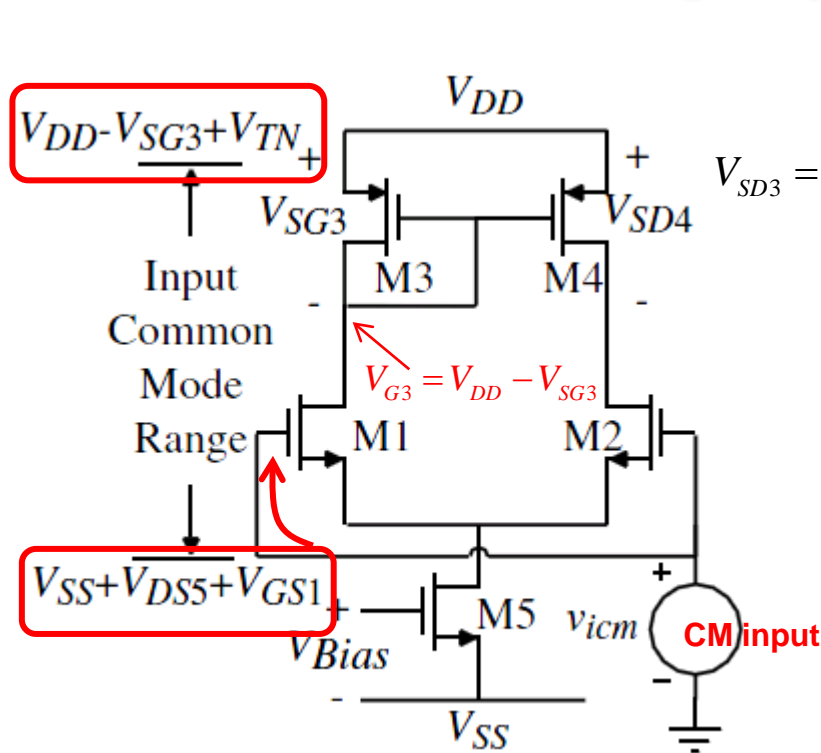

Diff amp. with a current mirror load

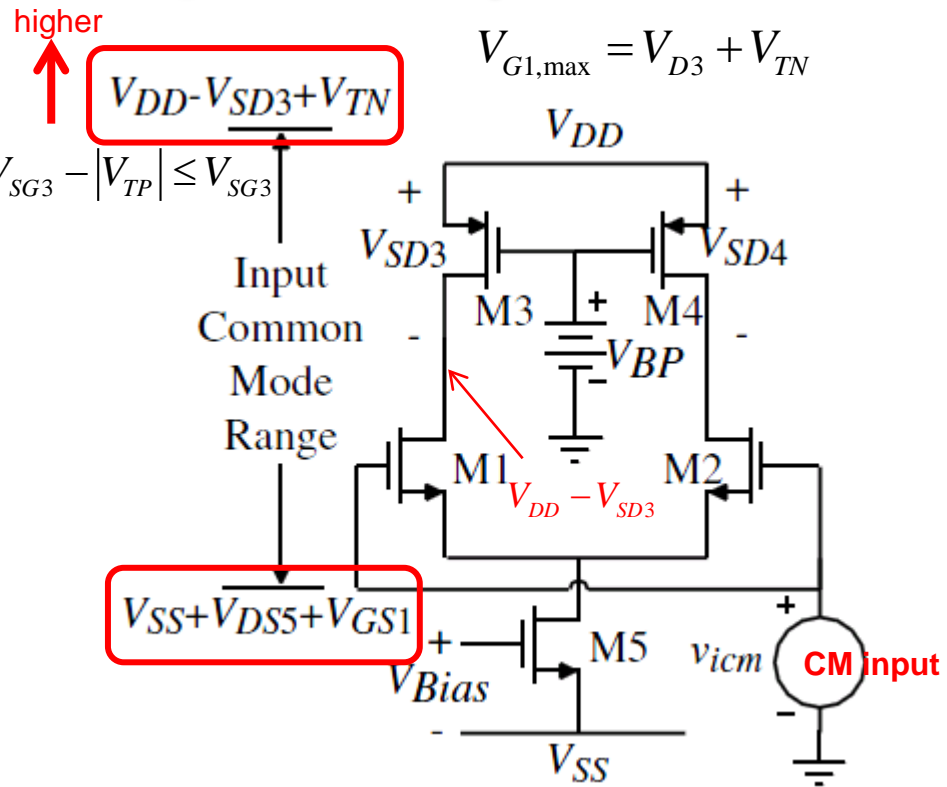


Diff amp. with a current source load

Using current source load has better ICMR.
 
# Gain and Phase Margins


- **Gain Margin (GM)**

- Gain of the amplifier at the point where the phase is  $180^\circ$ .
- **If this gain is larger than unity, the amplifier in closed-loop is unstable.**






- **Phase Margin (PM)**

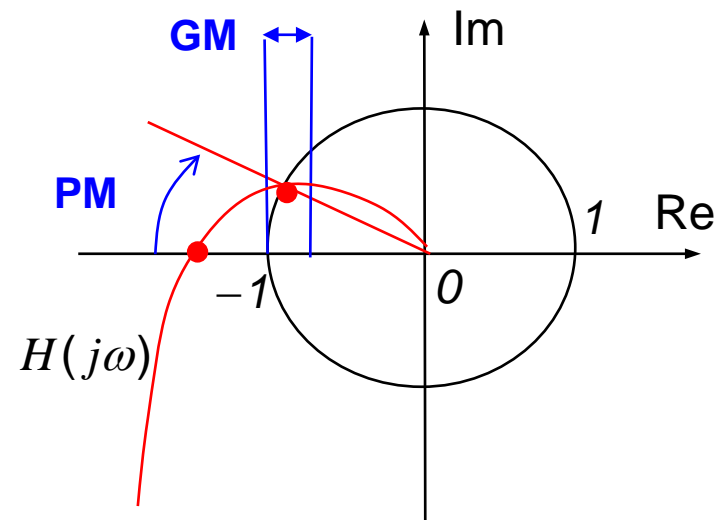- Difference between the phase at the unity gain (0dB) and  $180^\circ$ .
- **If the phase lag is greater than  $180^\circ$ , the amplifier in closed-loop is unstable.**


   
# Gain and Phase Margins

$$\frac{Y(s)}{U(s)} = \frac{H(s)}{1 + H(s)}$$






# Bandwidth (BW)

BW is measured at the point where gain falls by 3dB ( $0.707 = 1/\sqrt{2}$  of the max gain.)

Open-loop operation has extremely low BW.

 
**Closed-loop** significantly increases BW (but reduces the low-freq gain).



**Gain \* Bandwidth = GBW = Unity Gain Frequency**

**GBW is fixed hence specified in datasheet** while gain (depending on feedback) is set by the user.

# Freq-domain Metrics

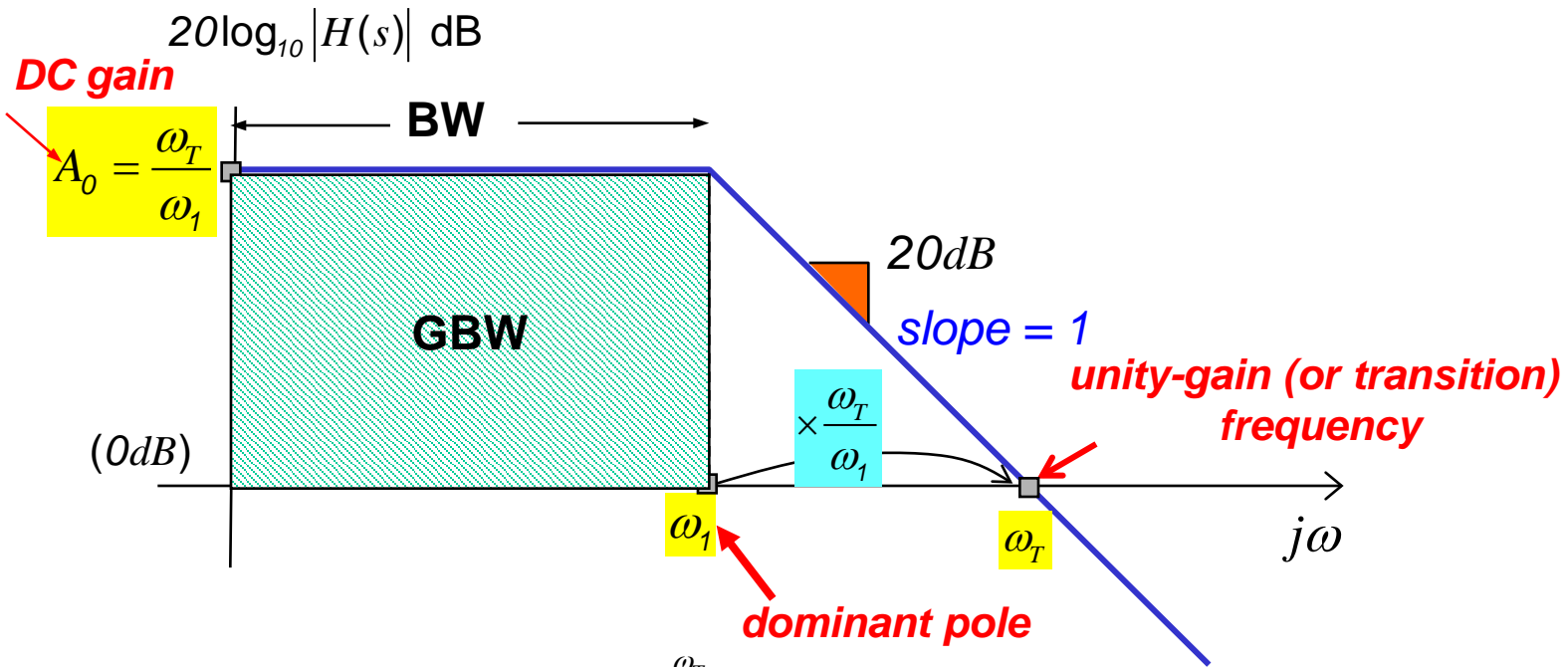

$$H(s) \approx \frac{\omega_T}{s + \omega_1} = \frac{\frac{\omega_T}{\omega_1}}{1 + \frac{s}{\omega_1}}$$


$$\frac{\omega_T}{\omega_1} \gg 1$$

**BW can be estimated by the dominant pole ( $s = -\omega_1$ ) and the DC gain.**

$$\text{GBW} = f_T$$

$$|H(s)|_{s=j\omega_T} = \frac{\frac{\omega_T}{\omega_1}}{\sqrt{1 + \left(\frac{\omega_T}{\omega_1}\right)^2}} \approx 1$$

# Open-loop, Closed-loop

 

Open-loop TF:  $A(s)$


$$A(s) \approx \frac{a}{1 + \frac{s}{p}} \quad \text{one-pole model}$$

Closed-loop TF:

$$A_{cl}(s) = \frac{V_o}{V_{in}} = \frac{A(s)}{1 + \beta A(s)} = \frac{\frac{a}{1 + \frac{s}{p}}}{1 + \frac{\beta a}{1 + \frac{s}{p}}} = \frac{a}{1 + \beta a + \frac{s}{p}}$$

$$A_{cl}(0) \approx \frac{1}{\beta} > 1 \quad \approx \frac{a}{\beta a + \frac{s}{p}}$$
 
$$\frac{1}{a} < \beta < 1 \quad \Rightarrow \quad \beta a > 1$$




The open-loop dc gain ( $a$ ) is large
 
# Slew Rate

Maximum rate of the output voltage rising/falling time.

$$SR = \frac{\Delta V_{OUT}}{\Delta t} \quad (V / \mu s)$$



It measures **how fast the output signal can “follow” the input signal.**

**\* We shall discuss in greater details on this subject in a later lecture.**

# *Simple Analog Design Tips*


# *Differential Circuit & Symmetry*

- Consider to use **differential** signal path
- **Differential circuit** has benefit of canceling noise and even-order nonlinear distortion
- Performance is limited by **matching** and **functional asymmetry** in the circuit,
  - bandgap, gm-C stages.
- Analog layout and routing should consider **symmetry** carefully.

 
# Signal-Path Devices

- **PMOS transistors have lower noise (whose mobility of holes is lower) comparing to NMOS**
  - Avoid using NMOS transistors in the signal path
- Consider to use balanced/symmetric **PMOS** devices on the signal path.

- **PMOS transistors** should be referenced to clean analog supply voltage.



 - **NMOS transistors** should be referenced to the substrate.





# *A Sample Opamp for Simulation*



# CMOS Opamp with Sizing

A sample opamp

 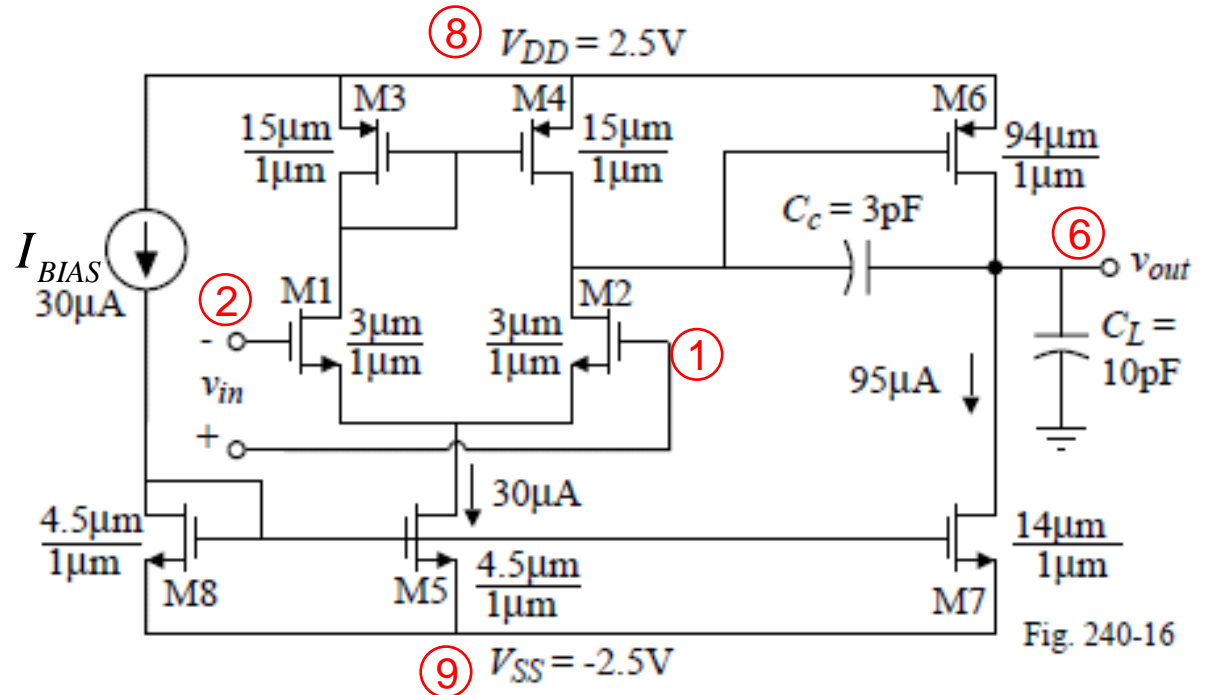

**Two-stage opamp with Miller compensation**

# Opamp Circuit

```
.SUBCKT OPAMP 1 2 6 8 9
M1 4 2 3 3 NMOS1 W=3U L=1U AD=18P AS=18P PD=18U PS=18U
M2 5 1 3 3 NMOS1 W=3U L=1U AD=18P AS=18P PD=18U PS=18U
M3 4 4 8 8 PMOS1 W=15U L=1U AD=90P AS=90P PD=42U PS=42U
M4 5 4 8 8 PMOS1 W=15U L=1U AD=90P AS=90P PD=42U PS=42U
M5 3 7 9 9 NMOS1 W=4.5U L=1U AD=27P AS=27P PD=21U PS=21U
M6 6 5 8 8 PMOS1 W=94U L=1U AD=564P AS=564P PD=200U PS=200U
M7 6 7 9 9 NMOS1 W=14U L=1U AD=84P AS=84P PD=40U PS=40U
M8 7 7 9 9 NMOS1 W=4.5U L=1U AD=27P AS=27P PD=21U PS=21U
CC 5 6 3.0P
.MODEL NMOS1 NMOS VTO=0.70 KP=110U GAMMA=0.4 LAMBDA=0.04 PHI=0.7
+MJ=0.5 MJSW=0.38 CGBO=700P CGSO=220P CGDO=220P CJ=770U CJSW=380P
+LD=0.016U TOX=14N
.MODEL PMOS1 PMOS VTO=-0.7 KP=50U GAMMA=0.57 LAMBDA=0.05 PHI=0.8
+MJ=0.5 MJSW=.35 CGBO=700P CGSO=220P CGDO=220P CJ=560U CJSW=350P
+LD=0.014U TOX=14N
IBIAS 8 7 30U
.ENDS
```

AD: Drain Area; PD: Drain Perimeter; (next page)

# Assignment 1

- Please simulate the sample opamp using your preferred simulator.
- Report the simulation results, including all modifications you made to the circuit.
- Also simulate the circuit in closed loop.
- Include both time-domain large-signal and frequency-domain small-signal simulation results.
- Due in one week. Please prepare to present!
- Submit printed report for grading. Remember to put in your name and student ID#.

# References

1. Prof. Yu, Sang Dae (劉尚大)'s Lecture, Kyungpook National University (韩国庆北大学), Integrated Systems Lab, School of Electronics Engineering, Taegu, Korea.
2. G. Palmisano, G. Palumbo, and S. Pennisi, “**Design procedure for two-stage CMOS transconductance operational amplifiers: a tutorial,**” Analog Integrated Circuits and Signal Processing, vol. 27, pp. 179-189, 2001.