

Lecture 5. Pole/Zero Analysis of Two-Stage Amplifiers

Prof. Guoyong Shi

shiguoyong@sjtu.edu.cn

School of Micro/Nano-electronics


Shanghai Jiao Tong University

2015

Outline

- Small-signal MOS models
- Two-stage opamp small-signal model
- Two-pole analysis
- Deriving poles and zeros by DPI
- Frequency compensation
- Design for phase margin
- **Pole/zero intuitions**
- Design strategies for zero
 - Canceling the 2nd pole by zero
 - Adding gain to the compensation path

Small-signal MOS Model

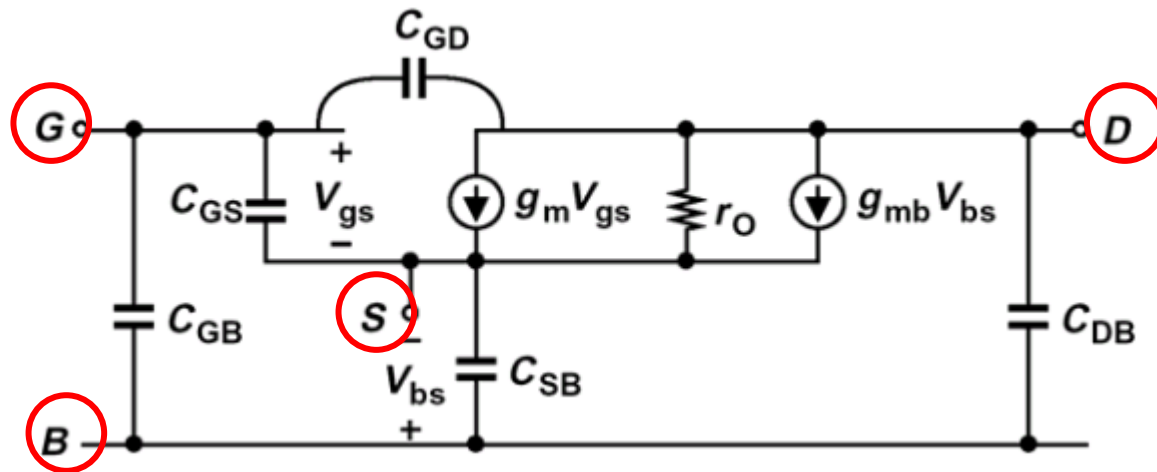


MOS Small-Signal Model

- G_m , G_{mb} , and G_o vary with the operation point.
- I_{ds} and V_{sb} are obtained by DC analysis.
- Other parameters are MOS device parameters.

$$g_o = \frac{\partial I_{ds}}{\partial V_{ds}} = \frac{1}{\lambda I_{ds}}$$

$$g_m = \frac{\partial I_{ds}}{\partial V_{gs}} = \sqrt{2kI_{ds} \frac{W}{L}}$$
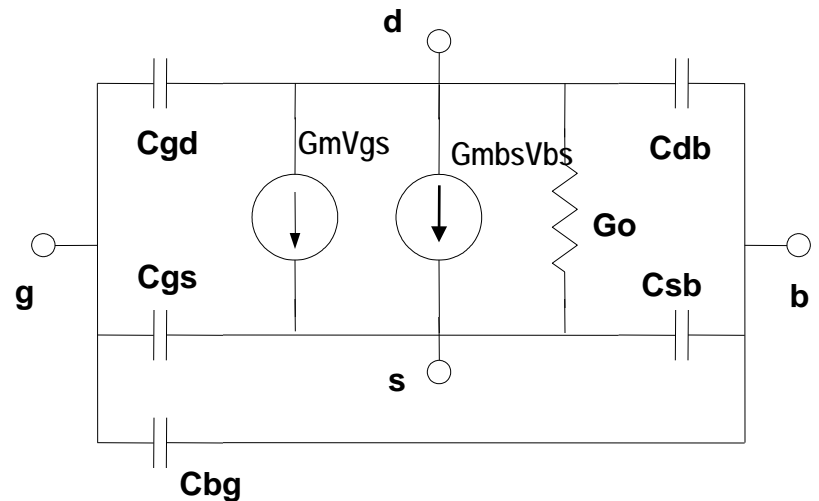
$$g_{mb} = \frac{\partial I_{ds}}{\partial V_{bs}} = \frac{\gamma}{2\sqrt{2\phi_f + V_{sb}}} g_m$$



Level 2 MOS Small-Signal Model


- C_{GS0} and C_{ox} etc. are the MOS device parameter.

$$C_{GS} = C_{GS0} + \frac{1}{2}C_{ox}$$


$$C_{GD} = C_{GD0} + \frac{1}{2}C_{ox}$$

$$C_{SB} = C_{JSB} + \frac{1}{2}C_{JBC}$$
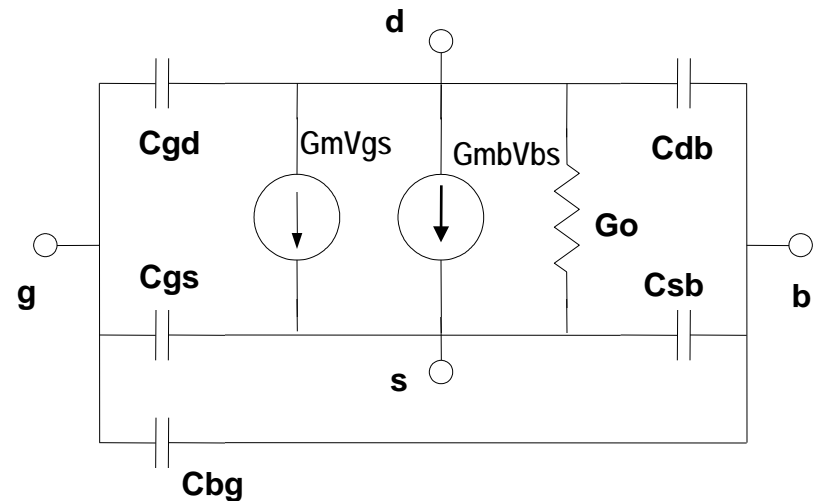
$$C_{DB} = C_{JDB} + \frac{1}{2}C_{JBC}$$





Level 3 MOS Small-Signal Model

 


NMOS


#Cap = 5
#Res = 5
#VCCS = 2

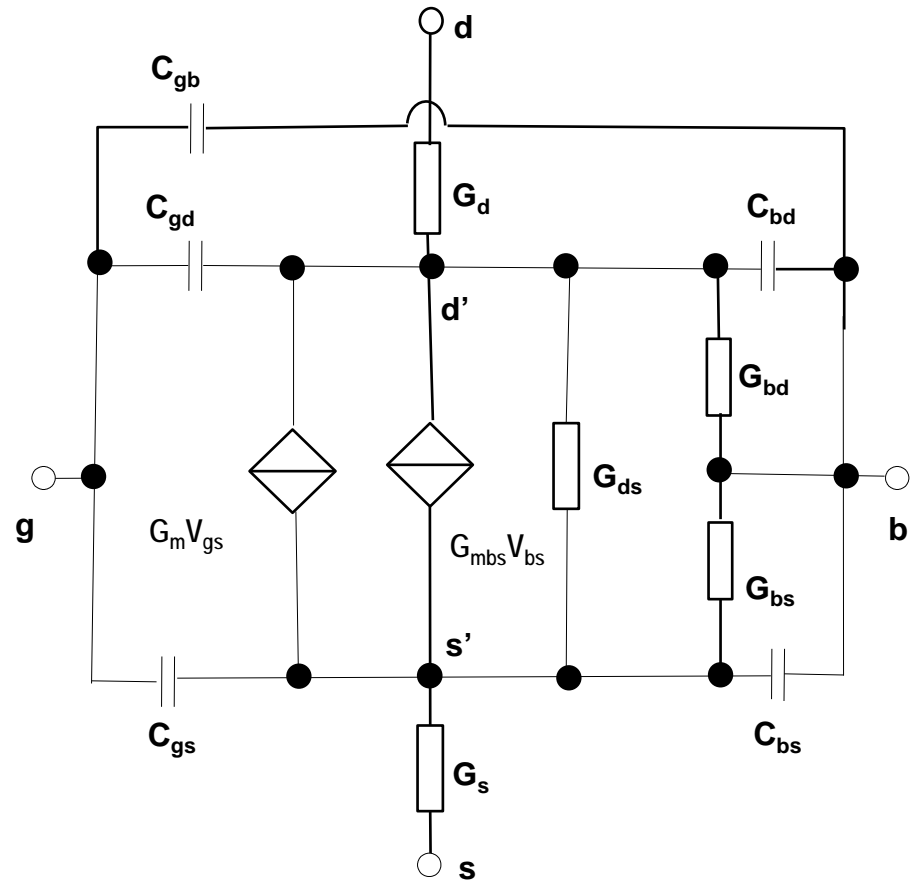 


Two-Stage Opamp (uncompensated)

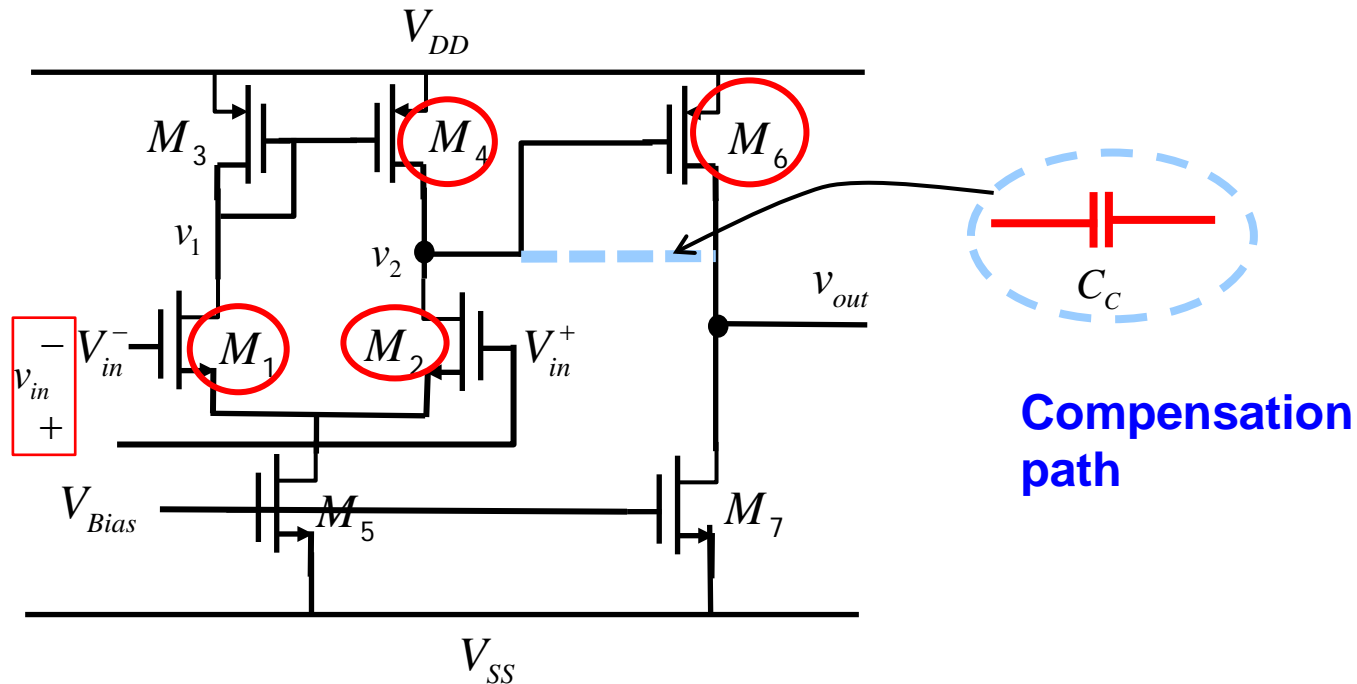

Small-signal model

 

Small-Signal Resistances

 


M3 diode connected

$$R_1 \approx r_{ds1} \parallel r_{ds3} \parallel \frac{1}{g_{m3}} \approx \frac{1}{g_{m3}}$$


$$R_2 = r_{ds2} \parallel r_{ds4}$$

$$R_3 = r_{ds6} \parallel r_{ds7}$$

Small-signal model

 

Parasitic Capacitances

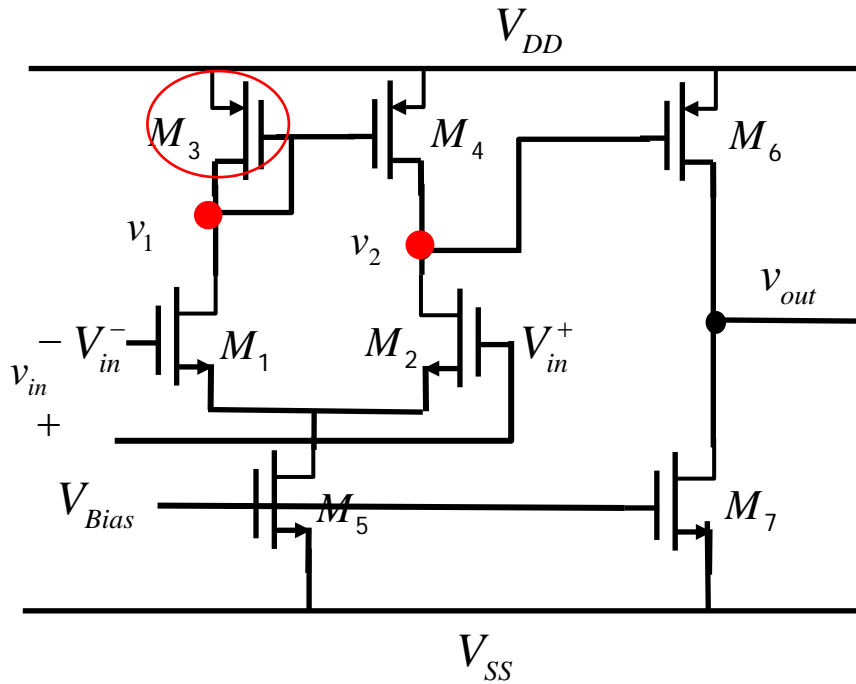


M3 diode connected

$$C_1 = C_{db1} + C_{gs3} + C_{db3} + C_{gs4}$$


$$C_2 = C_{db2} + C_{db4} + C_{gs6}$$

$$C_3 = C_{bd6} + C_{bd7} + C_L$$

Small-signal model

 

Simplified small-signal model

 

Assume:

$$C_1 \approx 0;$$

$$R_1 \approx \frac{1}{g_{m3}} \parallel r_{ds1} \parallel r_{ds3} \approx \frac{1}{g_{m3}}$$

(large)


$$v_1 = R_1 g_{m1} \frac{v_{in}}{2};$$

$$g_{m4} v_1 \approx g_{m4} \left(R_1 g_{m1} \frac{v_{in}}{2} \right) \approx \cancel{g_{m4}} \frac{1}{\cancel{g_{m3}}} g_{m1} \frac{v_{in}}{2} = g_{m1} \frac{v_{in}}{2}$$

$$R_2 = r_{ds2} \parallel r_{ds4}$$


$$R_3 = r_{ds6} \parallel r_{ds7}$$

(combine)

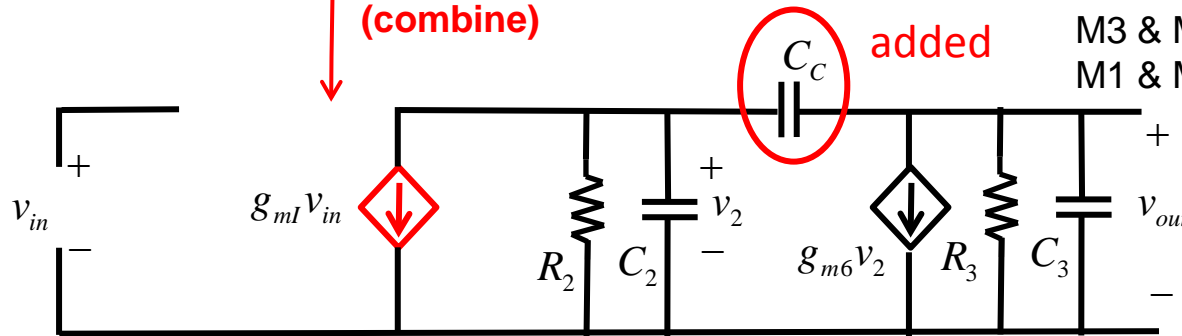

M3 & M4 are matched
M1 & M2 are matched

Simplified (Cont'd)

 


Subscripts I, II indicate the stages

$$g_{mI} = g_{m1} = g_{m2};$$

$$g_{mII} = g_{m6};$$

$$R_I = R_2 = r_{ds2} \parallel r_{ds4};$$
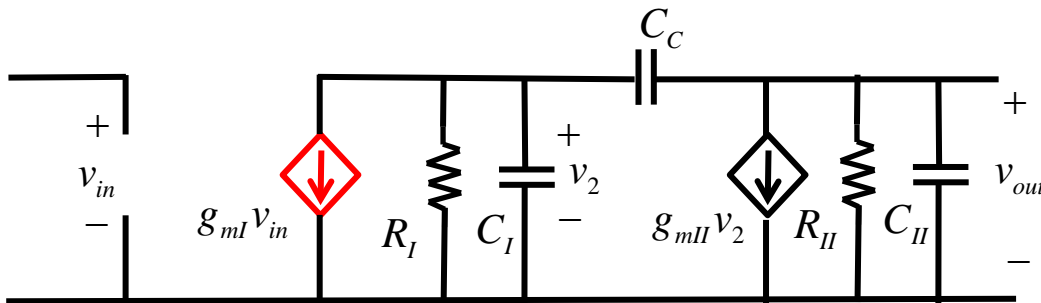
$$R_{II} = R_3 = r_{ds6} \parallel r_{ds7}$$




$$C_I = C_2 = C_{gs6} + C_{db2} + C_{db4}$$

$$C_{II} = C_3 = C_{db6} + C_{db7} + C_L \approx C_L$$


Assignment 2

- **Find the parasitic capacitances for the opamp circuit you used for SPICE simulation in the first assignment.**
- **Verify that the small-signal model has ac response close to the original circuit.**
- **Report any problems you have encountered.**


Driving Point Impedance (DPI)

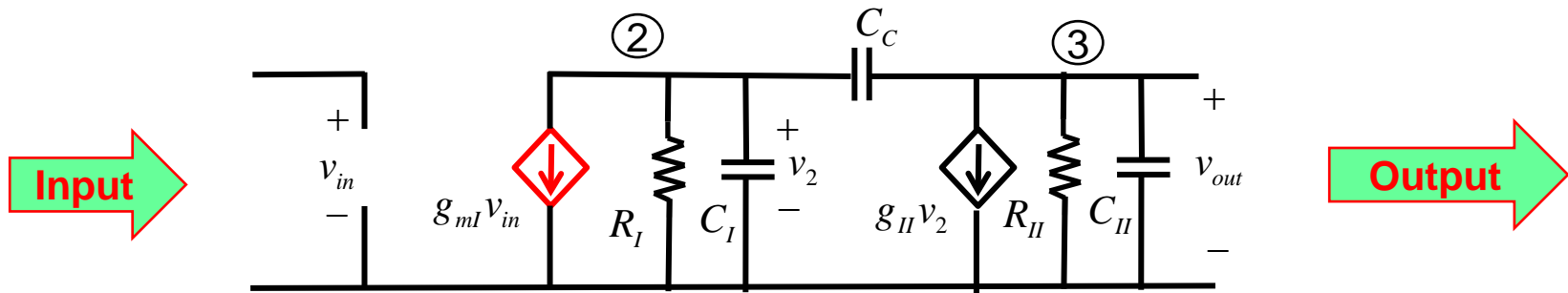

↓ To signal flow graph

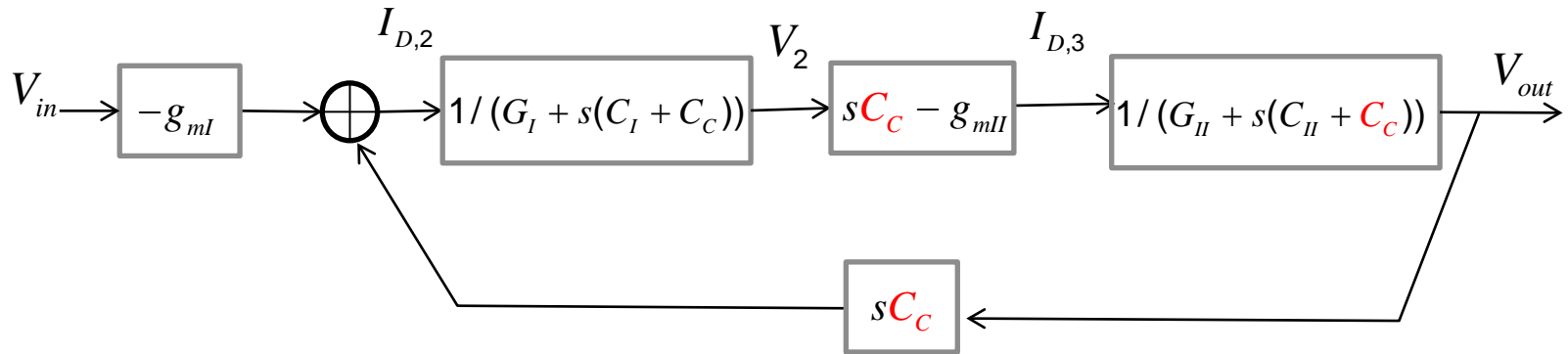

DPI-SFG Analysis

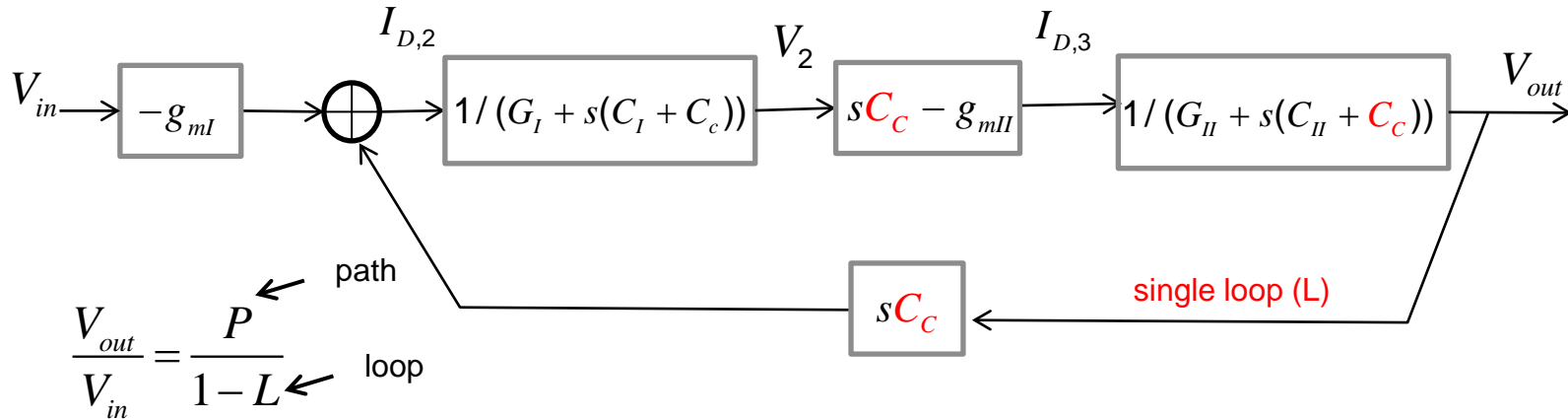

$$\begin{aligned}
 \frac{V_{out}}{V_{in}} &= \frac{g_{mI}(g_{mII} - sC_C)}{[G_I + s(C_I + C_C)][G_{II} + s(C_{II} + C_C)] - sC_C(sC_C - g_{mII})} \\
 &= \frac{A_0[1 - s(C_C / g_{mII})]}{1 + s[R_{II}(C_{II} + C_C) + R_I(C_I + C_C) + R_I R_{II} g_{mII} C_C] + s^2 R_I R_{II} [C_I C_{II} + C_C(C_I + C_{II})]}
 \end{aligned}$$



dc gain


$$A_0 = (R_I g_{mI})(R_{II} g_{mII})$$

one zero:

$$z = \frac{g_{mII}}{C_C} \text{ rad/s}$$

 
Exercise

Derive the expression for zero when a **nulling resistor** is added in the compensation path.



Poles
 
$$D(s) = \left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) = 1 - s \left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2}$$



$$D(s) \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$$

if $|p_2| \gg |p_1|$

(widely separated)

Approximately determine p_1 and p_2 by comparing to the polynomial $D(s)$:

$$D(s) = 1 + s \underbrace{[R_{II}(C_{II} + C_C) + R_I(C_I + C_C) + R_I R_{II} g_{mII} C_C]}_{-1/p_1} + s^2 \underbrace{R_I R_{II} [C_I C_{II} + C_C (C_I + C_{II})]}_{1/p_1 p_2}$$

Finding the Poles

$$D(s) = 1 + s \underbrace{[R_{II}(C_{II} + C_C) + R_I(C_I + C_C) + R_I R_{II} g_{mII} C_C]}_{-1/p_1} + s^2 \underbrace{R_I R_{II} [C_I C_{II} + C_C (C_I + C_{II})]}_{1/p_1 p_2}$$

(Dominating term)

$$p_1 = -1 / [R_{II}(C_{II} + C_C) + R_I(C_I + C_C) + R_I R_{II} g_{mII} C_C] \approx \frac{-1}{R_I R_{II} g_{mII} C_C} \quad (\text{for } g_{mII} \text{ large})$$

$$p_2 \approx \frac{-g_{mII} C_C}{C_I C_{II} + C_C (C_I + C_{II})} = \frac{-g_{mII} C_C}{(C_I + C_C) C_{II} + C_C C_I} \approx \frac{-g_{mII}}{C_{II}} \quad C_{II} \gg C_I$$

Note that the units of p_1 , p_2 are rad/s


Please take a look what transistors are related to these two poles?

The 2nd Pole


$$p_2 \approx \frac{-g_{mII} C_C}{C_I C_{II} + C_C (C_I + C_{II})} \approx -\frac{g_{mII}}{C_{II}}$$

$$C_{II} \gg C_C > C_I$$

 The **2nd pole** must be greater than GBW. Otherwise the phase margin might not be satisfied.



Frequency Compensation

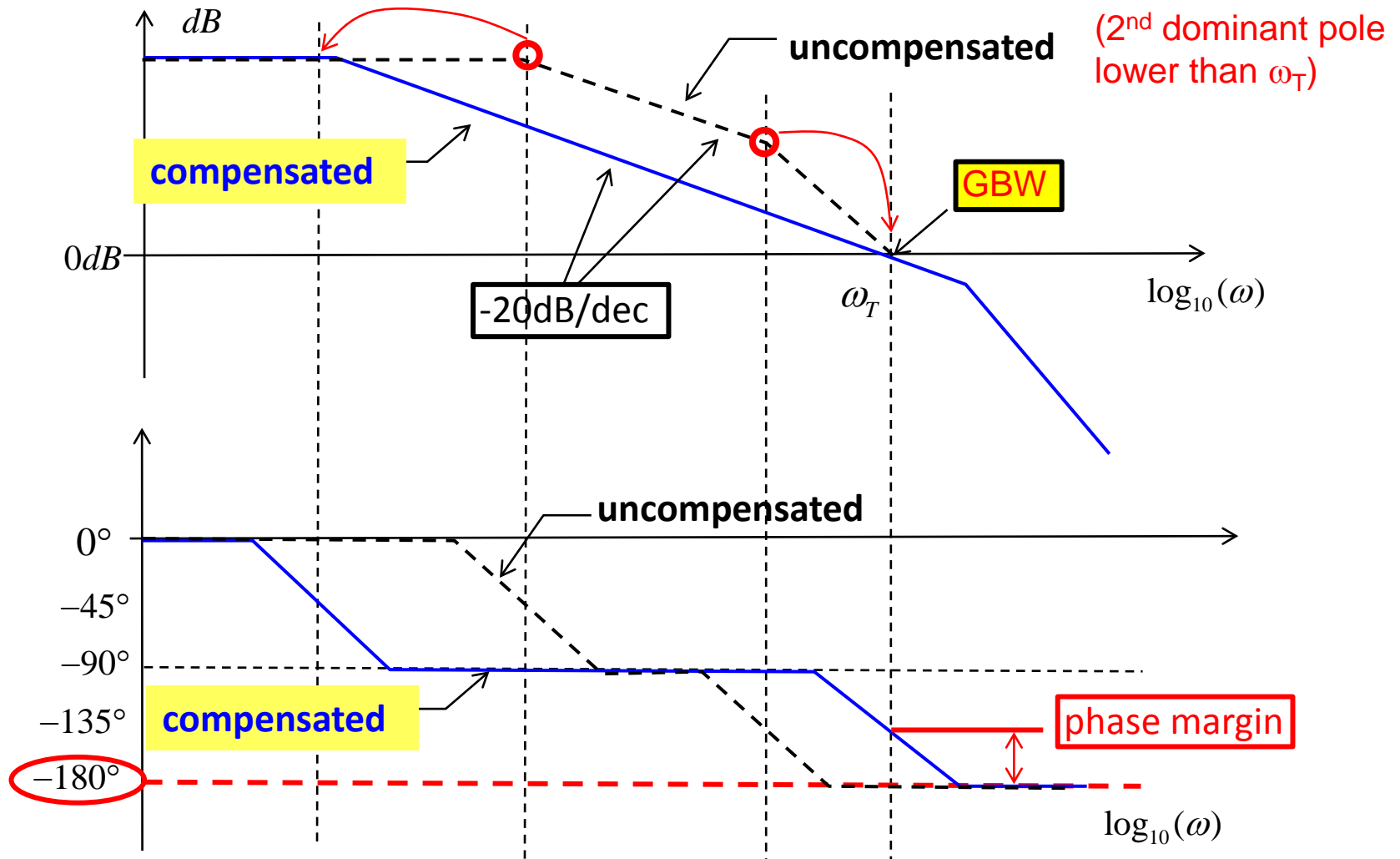

Gain-Bandwidth Product (GBW)


$$p_1 = -1 / [R_{II}(C_{II} + C_C) + R_I(C_I + C_C) + \overset{\text{(dominant)}}{R_I R_{II} g_{mII} C_C}] \approx \frac{-1}{R_I R_{II} g_{mII} C_C}$$

$$A_0 = (R_I g_{mI})(R_{II} g_{mII}) \quad \text{(dc gain)}$$

$$\Rightarrow GBW = A_0 |p_1| = \frac{(R_I g_{mI})(R_{II} g_{mII})}{R_I R_{II} g_{mII} C_C} = \frac{g_{mI}}{C_C} = \frac{g_{m1}}{C_C}$$

$$GBW = \frac{g_{m1}}{C_C}$$

Zero & Poles

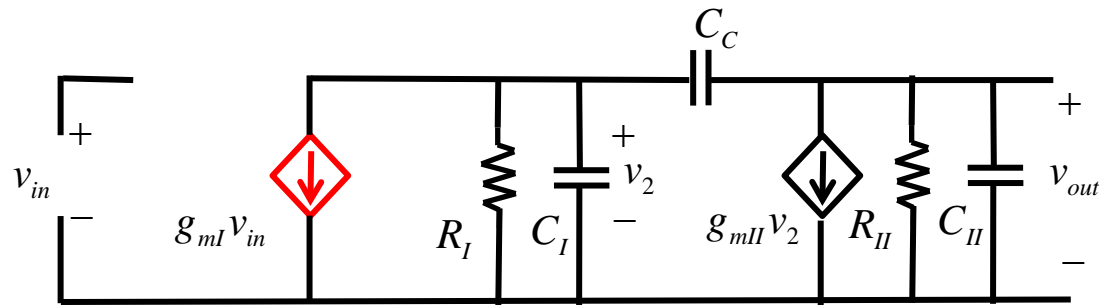

$$R_I = R_2 = r_{ds2} \parallel r_{ds4}; \quad R_{II} = R_3 = r_{ds6} \parallel r_{ds7} \quad g_{mII} = g_{m6};$$

Zero:

$$z = \frac{g_{mII}}{C_C} = \frac{g_{m6}}{C_C}$$

Poles:

$$p_1 \approx \frac{-1}{R_I R_{II} g_{mII} C_C} = \frac{-(g_{ds2} + g_{ds4})(g_{ds6} + g_{ds7})}{g_{m6} C_C}$$

$$p_2 \approx \frac{-g_{mII} C_C}{C_I C_{II} + C_C (C_I + C_{II})} \approx \frac{-g_{mII}}{C_{II}} \approx \frac{-g_{mII}}{C_L}$$

g_{mII} large

$C_{II} > C_C > C_I$

The output load C_L affects the 2nd pole.

Phase Margin

Open-loop transfer function $H(s)$:

$$H(s) = \frac{A_0(1 - s/z)}{(1 - s/p_1)(1 - s/p_2)} \quad z > 0; \quad p_{1,2} < 0$$

Phase:

$$\begin{aligned} \angle H(s) &= \angle(1 - s/z) - \angle(1 - s/p_1) - \angle(1 - s/p_2) \\ &= \varphi_z - \varphi_{p1} - \varphi_{p2} \in (0^\circ, -180^\circ) \end{aligned}$$

$$s = j\omega_T = jGBW$$


Suppose you want at least 45° phase margin:

$$\varphi_z - \varphi_{p1} - \varphi_{p2} > -180^\circ + 45^\circ = -135^\circ$$

$$\Rightarrow -\varphi_z + \varphi_{p1} + \varphi_{p2} < 135^\circ$$

$$\Rightarrow \tan^{-1} \frac{\omega_T}{z} + \tan^{-1} \frac{\omega_T}{|p_1|} + \tan^{-1} \frac{\omega_T}{|p_2|} < 135^\circ$$

 (The zero could be + or -.
A + zero worsens PM. Hence, called
"non-minimum phase zero".)



Design for Phase Margin

Placement of zero

$$\boxed{z > 10 \cdot GBW} \iff \frac{g_{m6}}{C_C} > \frac{10g_{m1}}{C_C} \iff \boxed{g_{m6} > 10g_{m1}}$$

$$\arctan \frac{GBW}{|z|} + \arctan \frac{GBW}{|p_1|} + \arctan \frac{GBW}{|p_2|} < 135^\circ$$

large $GBW = A_0 \cdot |p_1|$

Reference for sizing!

$$\Rightarrow \text{atan}(0.1) + 90^\circ + \text{atan}\left(\frac{GBW}{|p_2|}\right) < 135^\circ$$


$$\Rightarrow \text{atan}\left(\frac{GBW}{|p_2|}\right) < 45^\circ - 5.7^\circ = 39.3^\circ \Rightarrow \boxed{|p_2| \geq 1.22GBW}$$

Phase Marge (Alternative)


Alternatively, you may use **other estimates** to place the 2nd pole.

For example, **the CL also affects p2**, hence the phase margins.

$$C_C > 0.22C_{II}$$

 

$$|p_2| = \frac{g_{m6}}{C_{II}} > \frac{10g_{m1}}{C_{II}} > \frac{2.2g_{m1}}{C_C} = 2.2GBW$$

 

$$|p_2| \geq 2.2GBW$$


Pole/Zero Intuitions

- **Dominant pole**
- **Miller theorem**

The Dominant Pole

$$p_1 \approx \frac{-1}{R_I R_{II} g_{mII} C_C} = \frac{-1}{R_I \underbrace{[g_{mII} R_{II} C_C]}_{\text{Miller cap}}} \quad g_{mII} \text{ large}$$


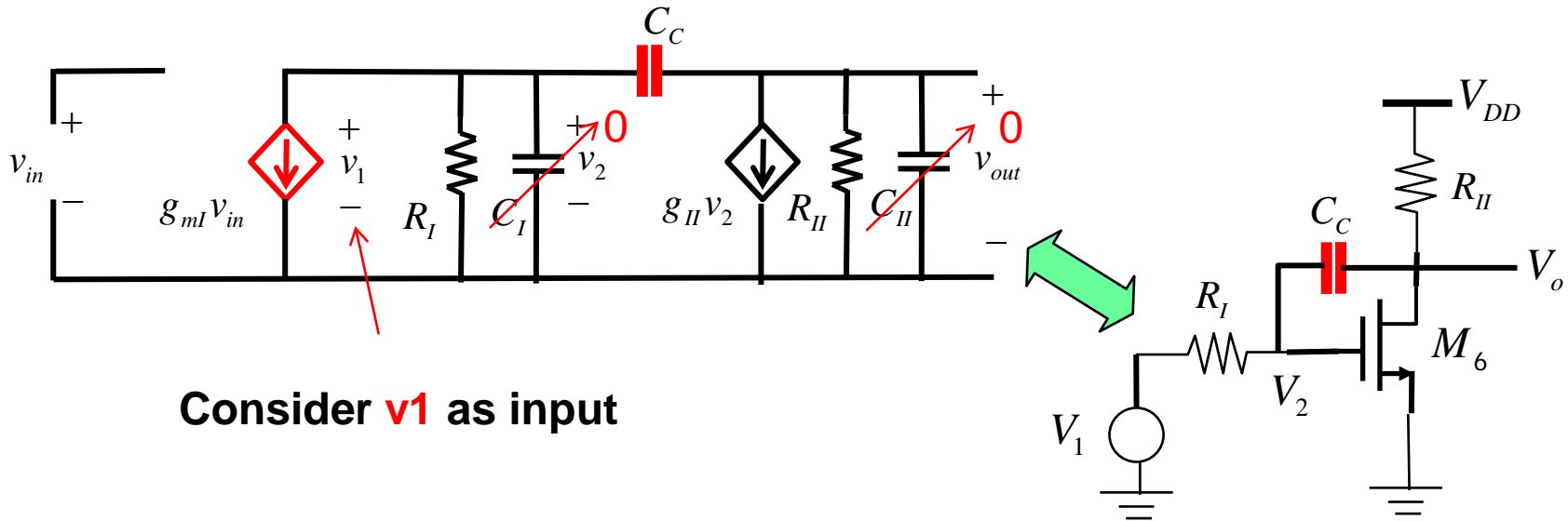
The **dominant pole (p1)** only depends on R_I , R_{II} , g_{mII} , and C_C , which is the pole of the following small-signal circuit:



Consider **v1** as input

Equiv. circuit

Approximate Treatment

 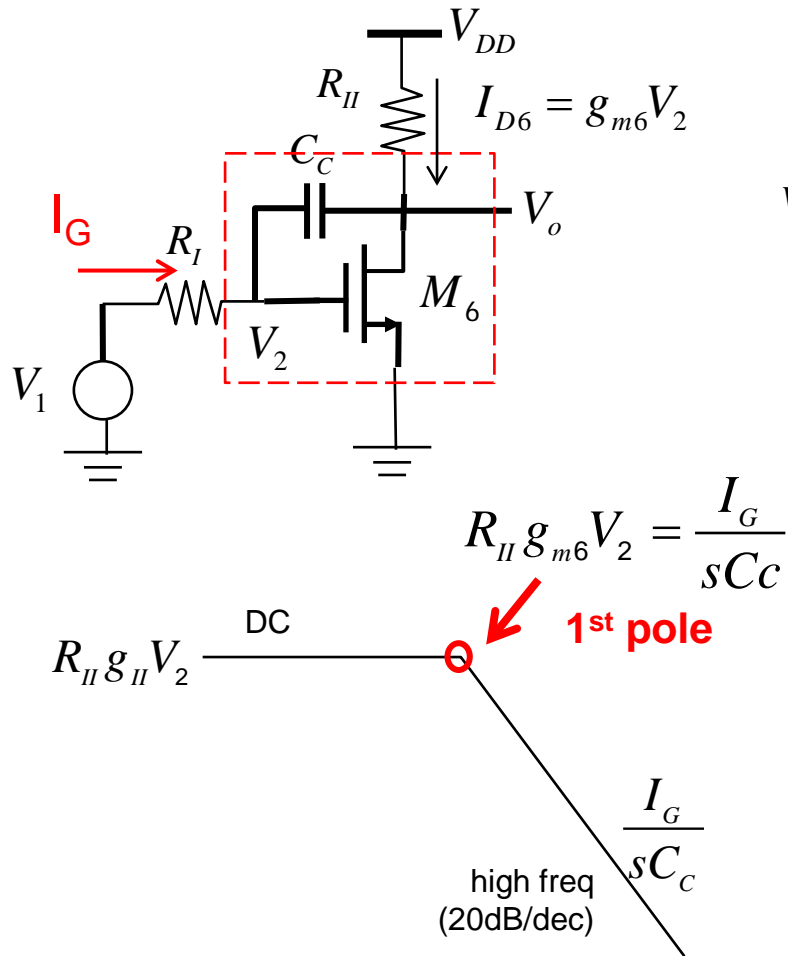

- At DC:


$$V_{out} = R_{II} g_{m6} V_2$$

- This circuit has a zero. Before reaching zero ($\omega C_C < g_{m6}$), the voltage drop at C_C dominates the output.


$$V_{out} = V_2 + \frac{I_G}{s C_C} \approx \frac{I_G}{s C_C}$$

One-pole Model

$$R_{II} g_{m6} V_2 = \frac{I_G}{sC_C}$$

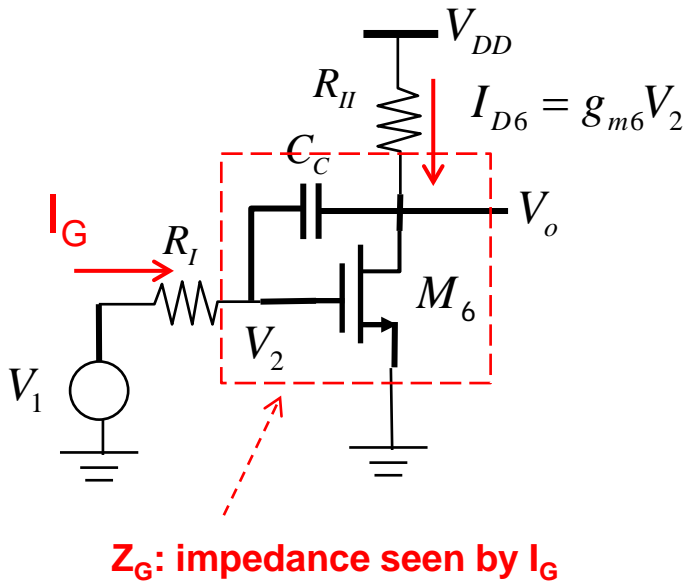

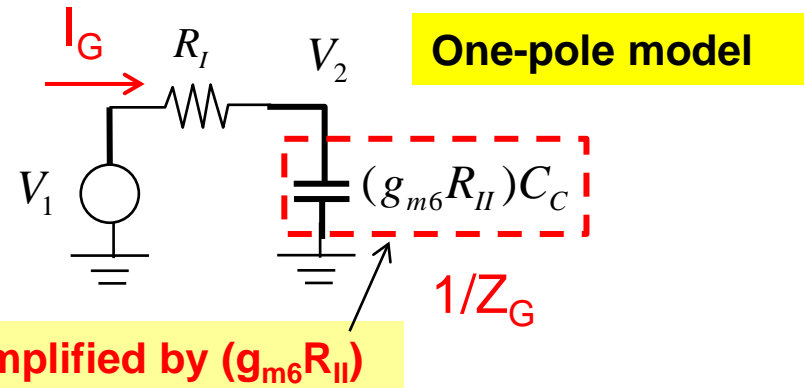
$$Z_G \equiv \frac{V_2}{I_G} = \frac{1}{sC_C g_{m6} R_{II}}$$



 Exercise

Derive the exact voltage transfer function by the DPI method.






$$\frac{V_o}{V_1} = \frac{(R_{II} g_{m6}) [1 - s(C_C / g_{m6})]}{1 + sC_C (R_I + R_{II} + R_I R_{II} g_{m6})}$$

Has a zero z and a pole p , $|z| > |p|$.

Dominant Pole
   
$$\frac{V_o}{V_1} = \frac{(R_{II} g_{mII}) [1 - s(C_C / g_{mII})]}{1 + sC_C (R_I + R_{II} + R_I R_{II} g_{mII})}$$



Dominant pole


$$p_1 \approx \frac{-1}{R_I (R_{II} g_{m6} C_C)}$$

Miller effect cap

Miller Theorem

Redistributing the feedback admittance to the two terminals

...

 


Proof

$$V_o = -AV_i; \quad A \gg 1$$


$$\left\{ \begin{array}{l} I_i = Y(V_i - V_o) = Y(1 + A)V_i \approx YAV_i; \quad I_i = Y_i V_i \\ I_o = Y(V_o - V_i) = Y(1 + \frac{1}{A})V_o \approx YV_o; \quad I_o = Y_o V_o \end{array} \right. \rightarrow \left\{ \begin{array}{l} Y_i \approx AY \\ Y_o \approx Y \end{array} \right.$$

Intuition of the 2nd Pole

 At high freq, **C_c is roughly short circuited**, M6 is almost **diode connected**.




$$C_{II} > C_C > C_I$$

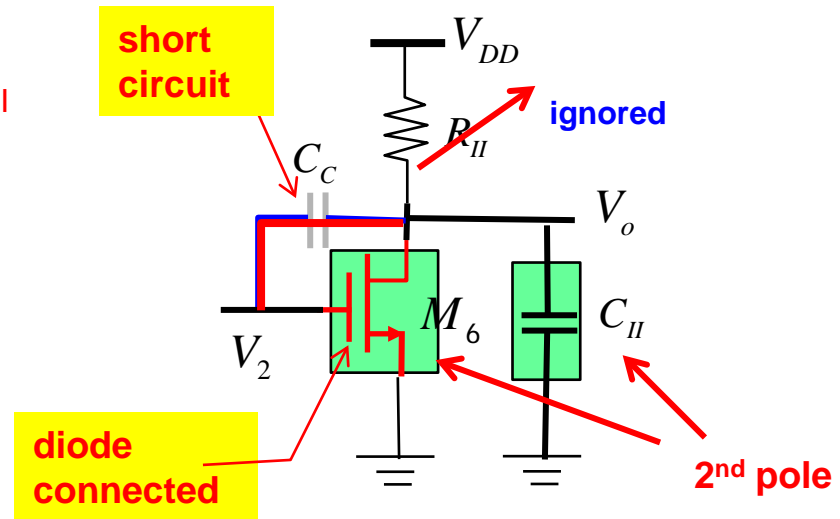


$$p_2 \approx \frac{-g_{mII}}{C_{II}} \quad (\text{indep of } C_c \text{ \& } R_{II})$$

The Mirror Pole

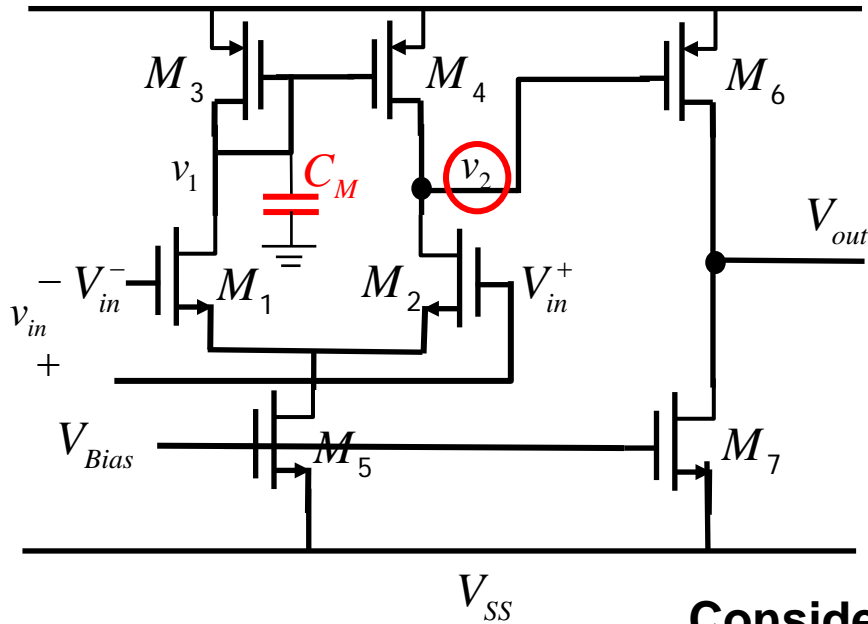


 C_M is the parasitic cap of the 1st stage mirror (it contributes to the **mirror pole**).




Consider transfer from v_{in} to v_2 .

(M3 is diode connected)

 


mirrored current in M4

 

Mirror Pole (cont'd)

Consider transfer from v_{in} to v_2 .

 

$$\begin{aligned}
 v_2 &= - \left[i_3 + \frac{g_{m2}v_{in}}{2} \right] \frac{1}{g_{ds2} + g_{ds4}} \\
 &= - \left[g_{m3}v_1 + \frac{g_{m2}v_{in}}{2} \right] \frac{1}{g_{ds2} + g_{ds4}} \\
 &= - \left[g_{m3} \frac{g_{m1}v_{in}}{2(g_{ds1} + g_{ds3} + g_{m3} + sC_M)} + \frac{g_{m2}v_{in}}{2} \right] \frac{1}{g_{ds2} + g_{ds4}} \quad (g_{m1} = g_{m2}) \\
 &= - \frac{g_{m1}}{2(g_{ds2} + g_{ds4})} \left[\frac{\text{small } g_{m3}}{\cancel{g_{ds1} + g_{ds3}} + g_{m3} + sC_M} + 1 \right] v_{in} \\
 &\approx - \frac{g_{m1}}{2(g_{ds2} + g_{ds4})} \left(\frac{2g_{m3} + sC_M}{g_{m3} + sC_M} \right) v_{in}
 \end{aligned}$$


These two roots are much larger (\gg GBW) \rightarrow their influence can be ignored.

Mirror zero: $z_M = -\frac{2g_{m3}}{C_M}$

Mirror pole: $p_M = -\frac{g_{m3}}{C_M}$

Zero Intuition

 Zero always arises from **superposition of multiple paths** from the input to output.



$$V_{o,1} = \frac{R_{II}}{(R_{II} + 1/sC_C)} V_1$$

R_{II} and C_C in series when driven by V_1

$$V_{o,2} = \frac{R_{II} / sC_C}{(R_{II} + 1/sC_C)} (-g_{m6}) V_2$$

R_{II} and C_C in parallel when driven by V_2

$$V_o = V_{o,1} + V_{o,2} = \frac{R_{II}}{(R_{II} + 1/sC_C)} V_1 + \frac{R_{II} / sC_C}{(R_{II} + 1/sC_C)} (-g_{m6}) V_2$$

Assuming $V_1 = V_2$

$$= \frac{R_{II} (1 - g_{m6} / sC_C)}{(R_{II} + 1/sC_C)} V_1$$

zero

$$z = \frac{g_{m6}}{C_C}$$

The Issue of Zero

A positive zero **boosts the magnitude** but **lags the phase**,

– i.e., **adding negative phase** to reduce the phase margin

Design Guide:


If the **zero is caused by two paths**, try to eliminate one path.

Design Strategies for Zero

- **Adding buffer to compensation path**
- **Adding output resistance of buffer**
- **Adding nulling zero**

Strategy 1

 
Adding **buffer** to break the compensation path




The **poles** are approximately **unchanged** (as if no buffer has been inserted).

Pole Analysis

No buffer

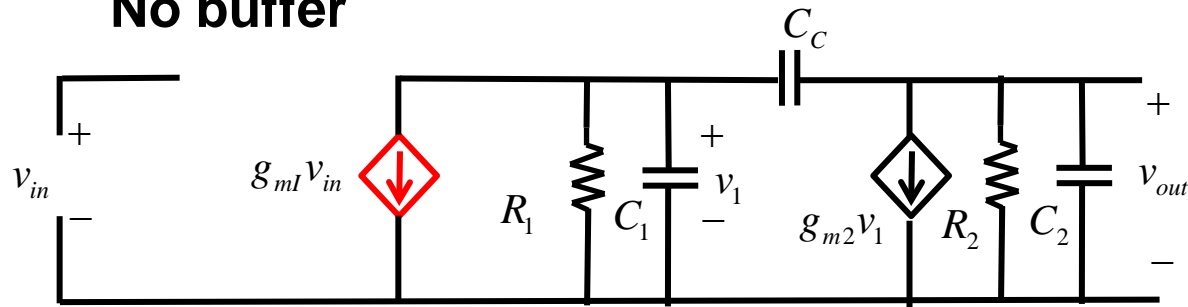


The two poles are unchanged

 

With buffer

$$p_1 \approx \frac{-1}{g_{m2} R_1 R_2 C_c}$$
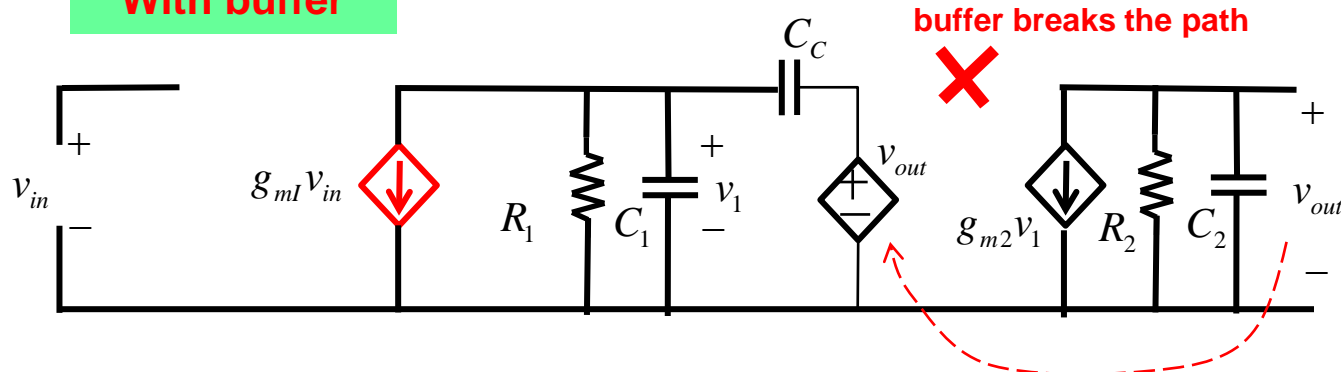
$$p_2 \approx \frac{-g_{m2} C_c}{C_2 (C_1 + C_c)}$$




buffer breaks the path



(buffer)

Strategy 2

Adding output resistance to buffer (R_b)

 

A **new pole** appears at

$$p_4 \approx \frac{-1}{R_b C_1 C_2 / (C_1 + C_c)}$$



and **additional LHP zero** at

$$z_2 = \frac{-1}{R_b C_c}$$


The **nulling resistor** placed in series with C_c can **eliminate** the RHP zero or move it to the LHP.

Exercise


Exercise: Derive poles-zeros for this circuit.

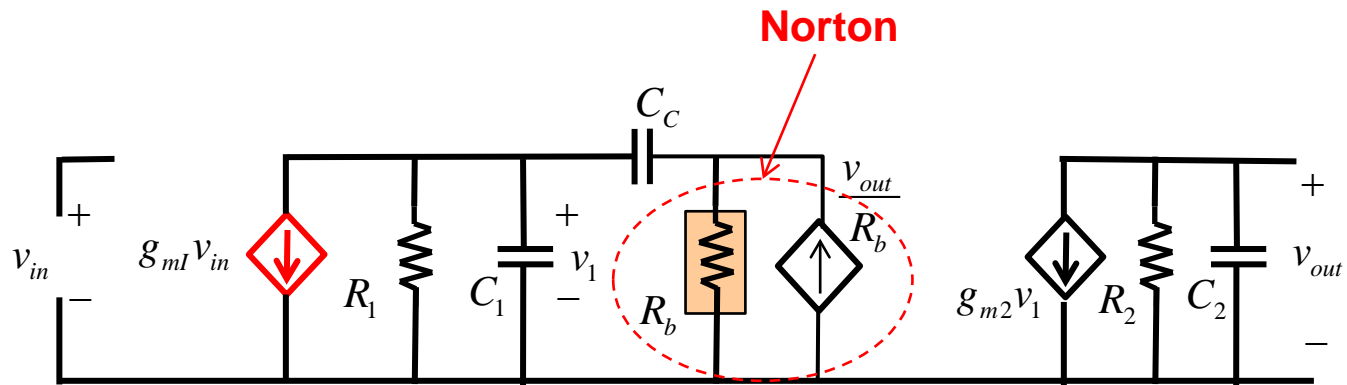 

Strategy 3: Nulling Resistor

 
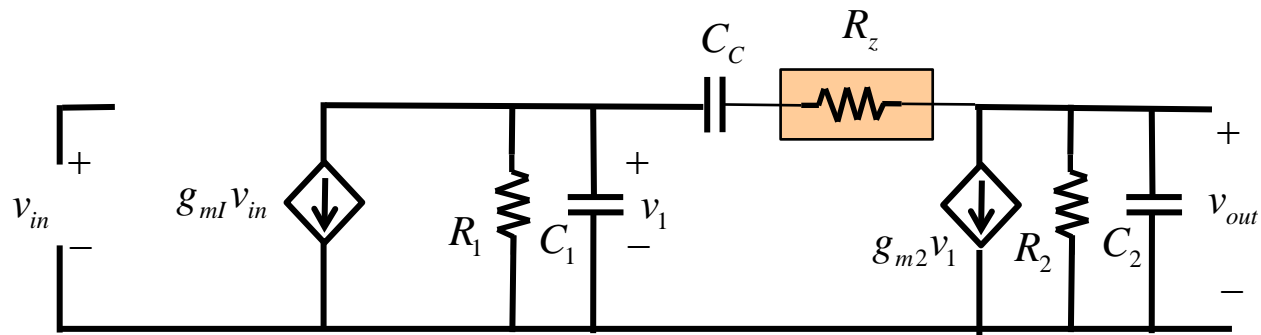
$$\frac{V_{out}}{V_{in}} = \frac{a \{1 - sC_c [1/g_{m2} - R_z]\}}{1 + bs + cs^2 + ds^3}$$



Exercise

Exercise: Derive the poles/zeros by DPI analysis.

$$\frac{V_{out}}{V_{in}} = \frac{a \{1 - sCc [1/g_{m2} - R_z]\}}{1 + bs + cs^2 + ds^3}$$

where the coefficients are:

$$a = g_{mI} g_{mII} R_I R_{II}$$

It becomes a 3rd order system

denominator

$$\left\{ \begin{array}{l} b = (C_{II} + C_C)R_{II} + (C_I + C_C)R_I + g_{mII}R_I R_{II} C_C + R_z C_C \\ c = R_I R_{II} (C_I C_{II} + C_C C_I + C_C C_{II}) + R_z C_C (R_I C_I + R_{II} C_{II}) \\ d = R_I R_{II} R_z C_I C_{II} C_C \quad \leftarrow \quad (3^{rd} \text{ order coeff}) \end{array} \right.$$

Note: subscripts I, II indicate stages 1 and 2.

Poles and Zero with nulling R_z

Assume R_z is less than R_I or R_{II} and the poles are widely spaced, then the roots are

$$p_1 = \frac{-1}{(1 + g_{mII} R_{II}) R_I C_C} \approx \frac{-1}{R_I C_C (g_{mII} R_{II})}$$


Exercise: Derive the poles and zero.

$$p_2 = \frac{-g_{mII} C_C}{C_I C_{II} + C_I C_C + C_{II} C_C} \approx \frac{-g_{mII}}{C_{II}}$$

$p_3 =$ mirror pole

$$p_4 = \frac{-1}{R_z C_I} \quad z_1 = \frac{1}{C_C \left(\frac{1}{g_{mII}} - R_z \right)} \approx \frac{1}{-C_C R_z} \quad (\text{if } g_{mII} R_z \gg 1)$$

Conceptual Illustration

 

$$V_{out} = \frac{R_{II}}{(R_{II} + R_z + 1/sC_C)} V_1 + \frac{(-g_{m6})R_{II}(R_z + 1/sC_C)}{(R_{II} + R_z + 1/sC_C)} V_2$$

$$= \frac{R_{II}(1 - g_{m6}R_z - g_{m6}/sC_C)}{(R_{II} + R_z + 1/sC_C)} V_1$$

Assuming $V_1 = V_2$


Assuming $g_{m6} = g_{mII}$, we get the zero as

$$z_1 = \frac{1}{C_C(1/g_{mII} - R_z)}$$

Zero Cancellation

If we place **z1 = p2**, i.e., let **the zero cancel the 2nd pole**.
 
$$\frac{1}{C_C (1/g_{mII} - R_z)} = \frac{-g_{mII}}{C_{II}}$$



$$\Rightarrow R_z = \frac{(C_C + C_{II})}{g_{mII} C_C}$$

With **p2 canceled**, the remaining roots are **p1 and p4 (p4 due to Rz)**. For unity-gain stability, it is required that


$$|p_4| > GBW = A_0 |p_1| = \frac{A_0}{g_{mII} R_I R_{II} C_C} = \frac{g_{mI}}{C_C} \Rightarrow |p_4| = \frac{1}{R_z C_I} > \frac{g_{mI}}{C_C} = GBW$$

Zero Cancellation (cont'd)

$$R_z = \frac{(C_C + C_{II})}{g_{mII} C_C} \approx \frac{C_{II}}{g_{mII} C_C}$$


$C_{II} \gg C_C$
 
$$\frac{1}{R_z C_I} > \frac{g_{mI}}{C_C} = GBW$$



substituting R_z
 
$$\frac{g_{mII} C_C}{C_I C_{II}} > \frac{g_{mI}}{C_C}$$




$$C_C > \sqrt{\frac{g_{mI}}{g_{mII}} C_I C_{II}}$$

This procedure gives **excellent stability** for a fixed value of C_2 ($\approx CL$).


Unfortunately, as **CL changes**, so does p_2 . Hence, the zero must be **adjusted** to cancel p_2 .

Pushing p2 Farther

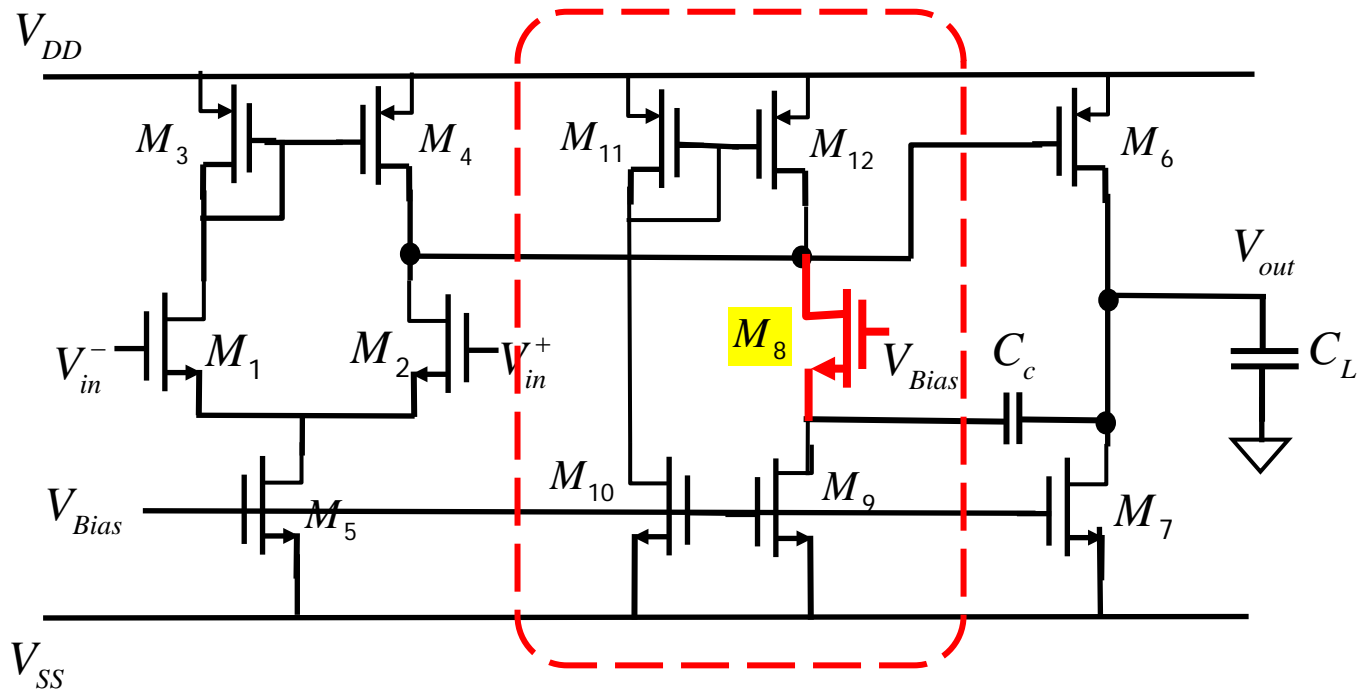
The magnitude of the **output pole (p2)** can be increased by **introducing gain in the feedback path of Miller capacitor (C_c)**.




Small-Signal Model

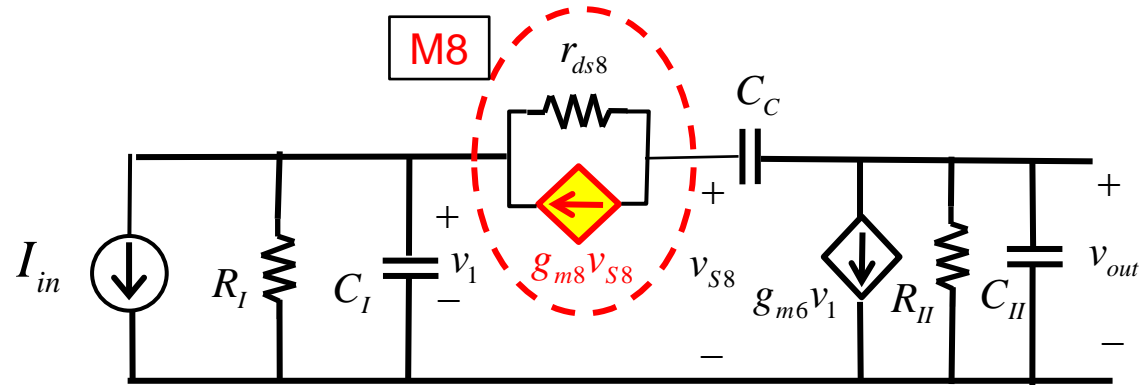


(equiv.)

 

$$r_{ds8} = 0$$

 

(cont'd)

 

The resistors R_I and R_{II} are defined as

$$R_I = \frac{1}{g_{ds2} + g_{ds4} + g_{ds12}} \approx \frac{1}{3g_{ds}} = \frac{r_{ds}}{3};$$

$$R_{II} = \frac{1}{g_{ds6} + g_{ds7}} \approx \frac{1}{2g_{ds}}$$

Assuming all the channel resistances are equal to r_{ds} .

Small-Signal Analysis

$$\frac{V_{out}}{I_{in}} = \left(\frac{-g_{m6}}{G_I G_{II}} \right) \frac{\left(1 + \frac{sC_C}{g_{m8}} \right)}{1 + s \left(\frac{C_C}{g_{m8}} + \frac{C_{II}}{G_{II}} + \frac{C_C}{G_{II}} + \frac{g_{m6} C_C}{G_I G_{II}} \right) + s^2 \left(\frac{C_C C_{II}}{g_{m8} G_{II}} \right)}$$

LHP zero \rightarrow

(Derived by DPI)

$\frac{1}{p_1 p_2}$

\Rightarrow Poles are

$$p_1 = \frac{-1}{\frac{C_C}{g_{m8}} + \frac{C_C}{G_{II}} + \frac{C_{II}}{G_{II}} + \frac{g_{m6} C_C}{G_I G_{II}}} \approx \frac{-6}{g_{m6} r_{ds}^2 C_C}$$

p_1 is roughly unchanged while the output pole has been multiplied by $(g_m r_{ds}/3)$.



$$G_I = 3r_{ds}^{-1}, G_{II} = 2r_{ds}^{-1}$$

$$p_2 \approx \frac{-g_{m6} r_{ds}^2 C_C}{6 \frac{C_C C_{II}}{g_{m8} G_{II}}} = -\frac{g_{m8} r_{ds}^2 G_{II} g_{m6}}{6 C_{II}} = -\frac{1}{3} g_{m8} r_{ds} |p_2'|$$


p_2' is the output pole of the regular Miller compensation

$$p_2' = -\frac{g_{mII}}{C_{II}} = -\frac{g_{m6}}{C_{II}}$$

Conceptual Interpretation

  


Output impedance of M6 is reduced

 

$$R_{out, M6} \approx \frac{1}{kg_{m6}} = \frac{3}{g_{m6}g_{m8}r_{ds}}$$

$$R_{out} \approx r_{ds7} \parallel \frac{3}{g_{m6}g_{m8}r_{ds8}} \approx \frac{3}{g_{m6}g_{m8}r_{ds8}}$$

(output pole) $|p_2| \approx \frac{g_{m6}g_{m8}r_{ds}}{3C_{II}}$

 

Remark: The **common gate M₈** stops the feedforward path, **preventing the occurrence of an RHP zero.**

$$z = -\frac{g_{m8}}{C_C}$$

Design Attempt (Assignment 3)

- Please attempt to modify the circuit structure of the 2-stage Miller-compensated opamp using the techniques learned in this lecture.
- You may attempt to use **one or two techniques introduced in this lecture.**
- Describe your attempts clearly in your turn-in.
- **Most likely your new design will fail ...**
- Then try to analyze why your new design fails, what are the main reasons you guess?
- In case you have observed improvement; try to analyze why and how such improvement is achieved.
- **Feel free to use the AICE tool.**
- **You are allowed to form 2~3 students as a working group by submitting one report.**

References

- P. E. Allen's lecture, ECE 6412, Analog Integrated Circuit Design –II, Georgia Tech, 2002.
- B. K. Ahuja, "An improved frequency compensation technique for CMOS operational amplifiers," *IEEE J. of Solid-State Circuits*, vol. SC-18, no. 6, Dec. 1983, pp. 629-633.
- G. Palmisano and G. Paumbo, "A compensation strategy for two-stage CMOS opamps based on current buffer," *IEEE Trans. Circuits Syst. I, Fundam. Theory Appl.*, vol. 44, no. 3, pp. 257–262, Mar. 1997.
- J. Mahattanakul and J. Chutichatuporn, "Design procedure for two-stage CMOS opamp with flexible noise-power balancing scheme," *IEEE Trans. Circuits Syst. I, Fundam. Theory Appl.*, vol. 52, no. 8, pp. 1508–1514, Aug. 2005.
- J. Mahattanakul, "Design procedure for two-stage CMOS operational amplifiers employing current buffer," *IEEE Trans. on CAS – II: Express Briefs*, vol. 52, no. 11, Nov. 2005.