

# Lecture 6

## Opamp Sizing

### (Part 1: Traditional Method)

**Prof. Guoyong Shi**

[shiguoyong@ic.sjtu.edu.cn](mailto:shiguoyong@ic.sjtu.edu.cn)

**Dept of Micro/Nano-electronics**

**Shanghai Jiao Tong University**

**2015**

# Outline

---

- Performance targets
- Sizing targets
- Opamp design procedure
  - Empirical procedure for manual sizing
- Techniques for enhancing GBW
  - Nulling resistor
  - Voltage buffer
  - Current buffer
- Sizing with voltage/current buffers

# Reference Paper

---

- This lecture was mainly based on the following paper:
- G. Palmisano, G. Palumbo, and S. Pennisi, “**Design procedure for two-stage CMOS transconductance operational amplifiers: a tutorial,**” Analog Integrated Circuits and Signal Processing, vol. 27, pp. 179-189, **2001**.

# Motivation

- Transistor sizing is one of the **most difficult** design stages **to automate** ;
- Sizing involves large / highly non-linear design space.
- So far, No fully automatic analog sizing tools are available for used either in industry or classroom.
- With manual design, **design space exploration** in the transistor weak and moderate inversion regions **becomes even harder**.

# List of Performance Targets

- Noise
  - Phase margin (PM or  $M_\phi$ )
    - If ( $M_\phi$ ) is not given, then **minimize the settling time.**
  - Gain-Bandwidth Product (GBW)
  - Load capacitance ( $C_L$ )
  - Slew rate (SR)
  - Input Offset Voltage
  - Input **Common Mode Range (CMR)**
  - Output Swing (OS)
  - **Common Mode Rejection Ratio (CMRR)**
  - **Power Supply Rejection Ration (PSRR)**
- } Not optimized during the manual design stage

# Comments on CMRR/PSRR

- Design parameters such as **dc gain, CMRR and PSRR**
  - depend on the MOS output resistance (**r<sub>ds</sub>**);
  - **They are not easily modeled for hand analysis.**
- These parameters highly **depend on the amplifier topology**.
  - For a **two-stage** opamp, typical **dc gain** in the range of **60-80dB (1,000x to 10,000x)**.
  - **CMRR** in the range of **70-90dB**.
  - They are predicted mainly by SPICE simulation **using accurate transistor models**.


# *Sizing Targets*

---

- **Biasing current**
- **Inversion levels**
- **Aspect ratios (W/L) of all transistors**
- **Compensation resistor ( $R_c$ ) / capacitor ( $C_c$ )**

**Palmisano, Palumbo and Pennisi (2001).**

# Two-stage Opamp

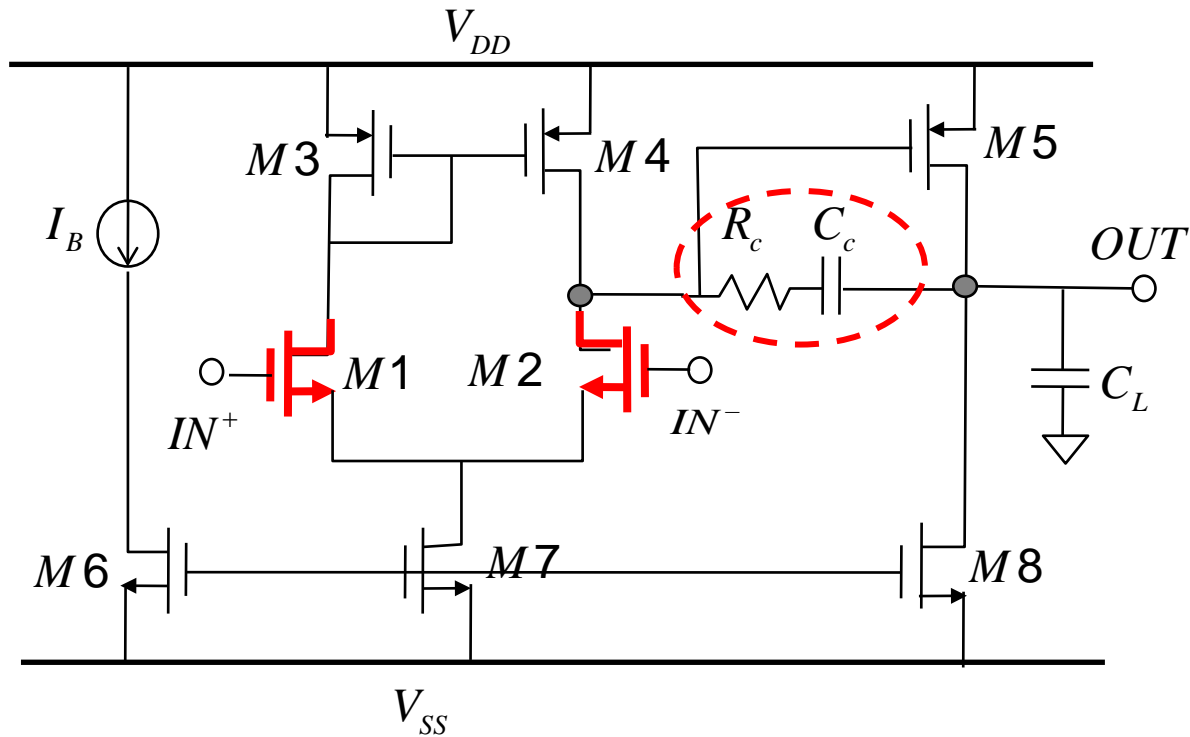


**Two-stage opamp (nMOS input)**


**Our working circuit in this course (2015)**



# Noise in Transistor

 
 
$$\overline{i_n^2} = 4kT \frac{2}{3} g_m \Delta f$$



**Useful Lemma:** The given two circuits are equivalent if  $\overline{V_n^2} = \overline{I_n^2} / g_m^2$

# Noise of Input Stage

Input referred noises (@ gate of M1):

1) Due to M3:


$$\overline{i_{n3}^2} = 4kT \frac{2}{3} g_{m3} \Rightarrow \overline{v_{n1 \leftarrow 3}^2} = \frac{\overline{i_{n3}^2}}{g_{m1}^2} = 4kT \frac{2}{3} \frac{g_{m3}}{g_{m1}^2}$$

2) Due to M1:

$$\overline{i_{n1}^2} = 4kT \frac{2}{3} g_{m1} \Rightarrow \overline{v_{n1}^2} = \frac{\overline{i_{n1}^2}}{g_{m1}^2} = 4kT \frac{2}{3} \frac{1}{g_{m1}}$$

Total IRN (two branches, doubled):
 
$$S_n(f) = 2 \times 4kT \frac{2}{3} \frac{1}{g_{m1,2}} \left( 1 + \frac{g_{m3,4}}{g_{m1,2}} \right)$$



# Design Procedure (by Palmisano et al.)

Step 1) Start from the noise requirement.

**Neglecting the flicker noise at low frequency**, the input noise voltage spectral density is given by

$$S_n(f) = 2 \times 4kT \frac{2}{3} \frac{1}{g_{m1,2}} \left( 1 + \frac{g_{m3,4}}{g_{m1,2}} \right) \quad (1)$$

To minimize noise, we assume (by sizing)  $g_{m3,4} \ll g_{m1,2}$  so that (1) is approximated by

$$g_{m1,2} \approx \frac{16}{3} \frac{kT}{S_n(f)} \quad (g_{m3,4} \ll g_{m1,2}) \quad \Rightarrow$$


So, noise spec determines  $g_{m1,2}$

The **low frequency flicker noise** can be lowered by **increasing L** and **W** of M1 and M2 (the input pair).

# Compensation Capacitor ( $C_c$ )

Step 2) The **compensation capacitor ( $C_c$ )** is determined by  $g_{m1,2}$  and the **GBW requirement**:

$$\omega_T = \frac{g_{m1,2}}{C_c}$$

 

$$C_c = \frac{g_{m1,2}}{\omega_T} = \frac{g_{m1,2}}{2\pi f_T}$$

# Slew Rate

- **Step 3)** The slew rate depends on two part:
- -- the slew at the **output node of the 1<sup>st</sup> stage (internal slew rate)**
- -- and slew at the **output node of the 2<sup>nd</sup> stage (external slew rate)**.

The slew rates are related to the **quiescent currents**  $I_{D1,2}$  (input stage) and  $I_{D8}$  (output stage) :

$$SR_{int} = \frac{2I_{D1,2}}{C_C} = \frac{I_{D7}}{C_C};$$

(internal)

$$SR_{ext} = \frac{I_{D8} - I_{D7}}{C_L}$$

(external)

In practice, we would set both **internal and external SR's**  $\geq$  **target SR.**

However, at the beginning let us set:  **$SR_{int} = SR_{ext} = SR.$**


# SR (cont'd)

(external)


$$SR = \frac{I_{D8} - I_{D7}}{C_L}$$

(internal)

 
$$SR = \frac{2I_{D1,2}}{C_C} = \frac{I_{D7}}{C_C};$$


 
$$C_L SR = I_{D8} - C_C SR \quad \leftarrow \quad I_{D7} = C_C SR$$



$$SR = \frac{I_{D8}}{C_C + C_L}$$

 

$$I_{D8} = SR(C_C + C_L) = \frac{(C_C + C_L)}{C_C} I_{D7}$$

which determines the current ratio between  $I_{D8}$  &  $I_{D7}$ .

# Sizing M1,2

## Step 4) Size the input transistors.

$$I_D = \frac{\beta}{2} [2(V_{GS} - V_T) - V_{DS}] V_{DS};$$

$$\beta = \mu C_{ox} \frac{W}{L} = K_{n,p} \frac{W}{L}$$

$$I_{DSAT} = \frac{\beta}{2} (V_{GS} - V_T)^2 = \frac{\beta}{2} (V_{DSAT})^2$$

$$K_{n,p} = \mu C_{ox}$$

$$g_m = \frac{\partial V_{DSAT}}{\partial I_{DSAT}} = \beta V_{DSAT} = \sqrt{2\beta I_{DSAT}} = \sqrt{2K_{n,p} \frac{W}{L} I_{DSAT}}$$

Use this gm equation for sizing

$$\frac{W}{L} = \frac{g_m^2}{2K_{n,p} I_{DSAT}}$$

$g_m$  and  $I_D$  determine the size ratio

Recall that gm1,2 was determined by the noise spec.

# Phase Margin


## Step 5) Determine the phase margin.

- For 2-stage amplifier, the first two poles,  $p_1$  and  $p_2$  can approximately characterize the frequency behavior.

Two-pole approximation of the open-loop  $H(s)$ :

$$H(s) = \frac{A}{\left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right)}$$

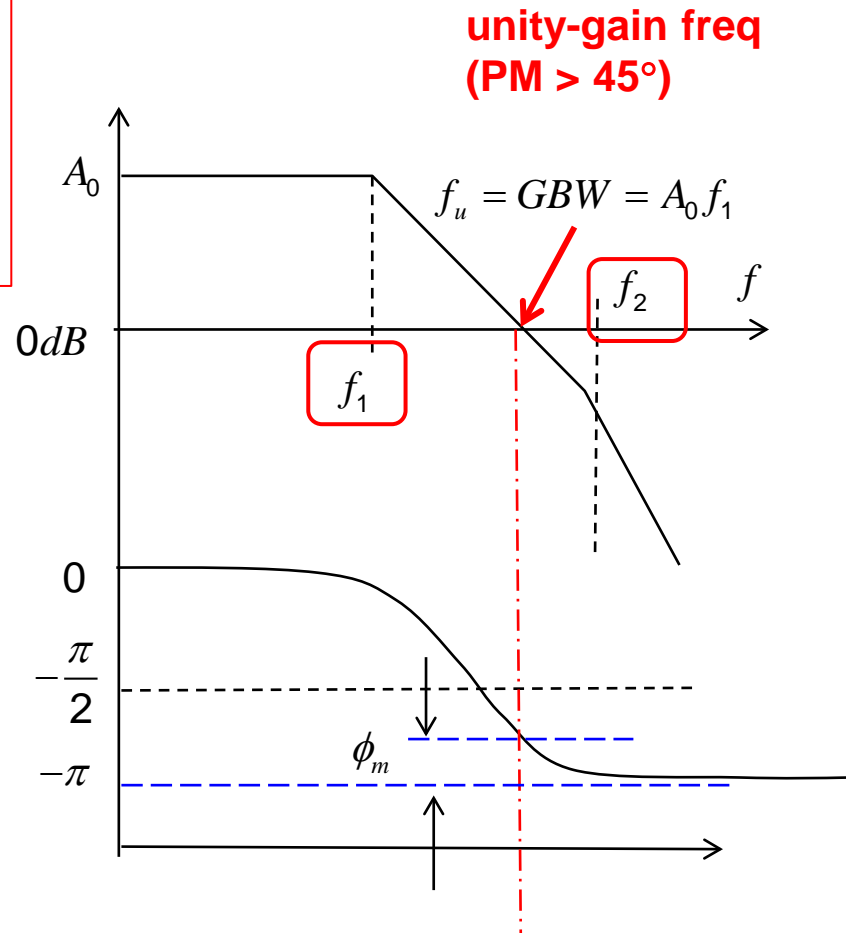⇒ 
$$H(jf_u) = \frac{A}{\left(1 + \frac{jf_u}{f_1}\right)\left(1 + \frac{jf_u}{f_2}\right)}$$





# Phase Margin (cont'd)

For **PM > 45°**, we may approximate  **$f_u = \text{GBW}$** .

$$\begin{aligned} \Rightarrow \angle H(j\omega_u) &= -\tan^{-1} \frac{f_u}{f_1} - \tan^{-1} \frac{f_u}{f_2} \\ &= -\tan^{-1} \underbrace{\frac{f_1 \cdot A_0}{f_1}}_{\approx \pi/2} - \tan^{-1} \frac{f_u}{f_2} \approx -\frac{\pi}{2} - \tan^{-1} \frac{f_u}{f_2} \end{aligned} \quad (\text{gain } A_0 \gg 1)$$

$$\Rightarrow \angle H(j\omega_u) \approx -\frac{\pi}{2} - \tan^{-1} \frac{f_u}{f_2}$$

GBW & p2  
determine the  
PM

$$\Rightarrow \text{Phase margin: } \phi_m = \angle H(j\omega_u) - (-\pi)$$

$$\phi_m = \pi + \angle H(j\omega_u) \approx \frac{\pi}{2} - \tan^{-1} \frac{f_u}{f_2} \quad \leftarrow \text{2nd pole}$$

# Phase Margin and Poles


The **phase margin (PM)** is given by:

$$\phi_m = \frac{\pi}{2} - \arctan \frac{GBW}{f_2}$$

$$f_u = GBW$$

$$p_i = -2\pi f_i$$


**2<sup>nd</sup> pole**

 

$$\tan \phi_m = \frac{f_2}{GBW} \triangleq \chi$$

(called “**separation factor**”  
introduced by Palmisano &  
Palumbo 1998)

 The **2<sup>nd</sup> pole** occurs at:  $2\pi f_2 = \frac{g_{m5}}{C_L}$



$$g_{m5} = 2\pi f_2 C_L = 2\pi C_L (GBW) \tan \phi_m$$

**Size M5 by GBW &  
PM**

**Step 6) Determine gm5, then the size of M5.**

G. Palmisano and G. Palumbo, “A novel representation for two-pole feedback amplifiers,” *IEEE Trans. on Education*, vol. 41, no. 3, Aug. 1998, pp. 216-218.

# Compensation Capacitor ( $C_c$ )

The “separation factor”  $\chi$ :

$$\chi \triangleq \tan \phi_m = \frac{f_2}{GBW} = \frac{f_2}{f_u} \quad (\text{holds for PM} > 45^\circ)$$

Recall the 2<sup>nd</sup> pole & GBW:

$$f_2 = \frac{g_{m5}}{2\pi C_L}, \quad f_u = \frac{g_{m1,2}}{2\pi C_c}$$

⇒ 
$$\chi = \frac{f_2}{f_u} = \frac{g_{m5}}{g_{m1,2}} \frac{C_c}{C_L}$$

⇒ 
$$C_c = \chi \frac{g_{m1,2}}{g_{m5}} C_L$$

Use the separation factor to determine  $C_c$


**Step 7):** Choose a separation factor  $\chi$  (say, 2) to determine  $C_c$ .

# Sizing M5

Since  $I_{D5} = I_{D8}$ , the size of M5 is given by

$$\left(\frac{W}{L}\right)_5 = \frac{g_{m5}^2}{2KI_{D5}}$$

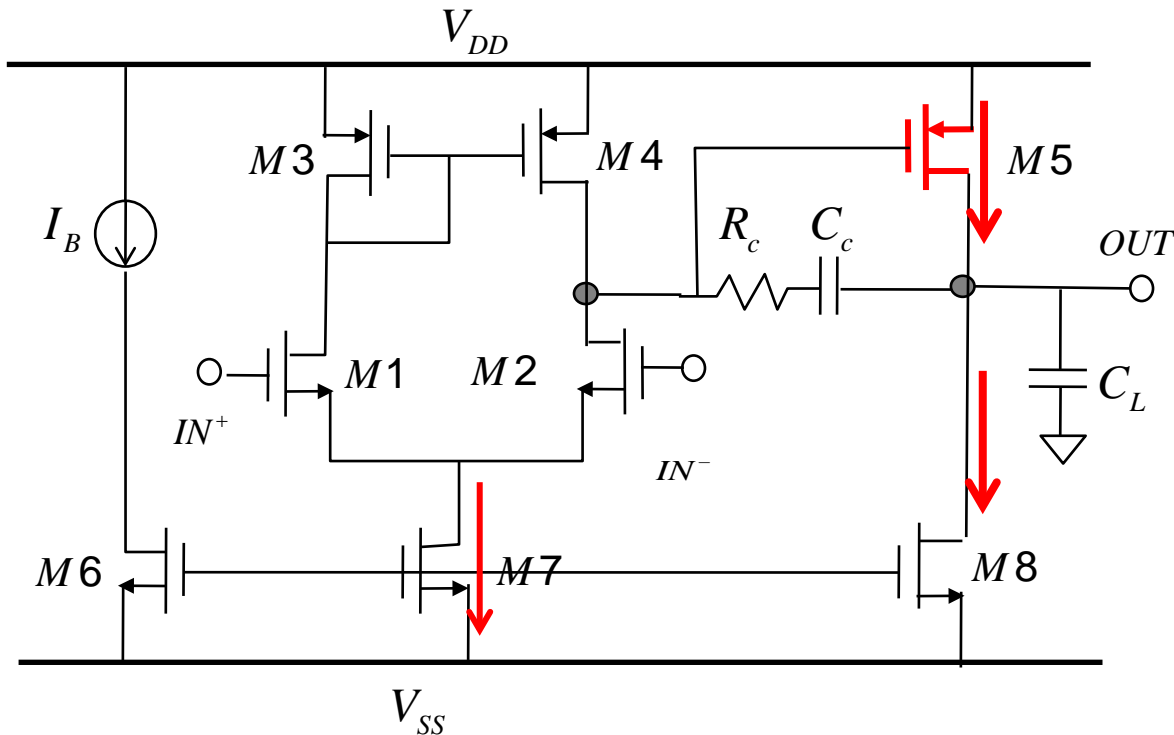$I_{D7}$  &  $I_{D8}$  were determined by SR (step 3).



# *Design for Better Bandwidth*

With the previous method, the maximum achievable GBW is limited by the 2<sup>nd</sup> pole  $p_2 = -g_{m5}/C_L$ , which depends on the load capacitor  $C_L$ .

To achieve a higher GBW, a **very high  $g_{m5}$**  is required.

Optimize GBW **with minimum change of the remaining** electrical parameters.

# Nulling Resistor

The **left half-plane (LHP) zero** introduced by the **nulling resistor  $R_c$**  is

$$f_z = \frac{1}{2\pi} \frac{g_{m5}}{(1 - g_{m5} R_c) C_C}$$

Setting  $R_c = 1/g_{m5}$  pushes the RHP zero to **infinity**.

Further increasing  $R_c$  flips over the zero into LHP.

# Pole-zero Cancellation

$$f_z = \frac{1}{2\pi} \frac{g_{m5}}{(1 - g_{m5} R_z) C_z} = f_2 = -\frac{g_{m5}}{2\pi C_L} \quad (1)$$


We shall determine  $C_z$  and  $R_z$  .

Insertion of the nulling resistor ( $R_C$ ) results in **the new (3<sup>rd</sup>) pole:**

$$f_3^{new} = \frac{1}{2\pi R_z C_I}, \quad C_I = C_{db2} + C_{db4} + C_{gs5}$$

Cap load of 1<sup>st</sup> stage

Again, define the new **separation factor**
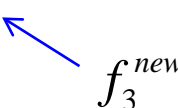
$$\chi = \frac{f_3^{new}}{f_{GBW}} = \frac{C_C}{g_{m1,2} R_C C_I} \quad (2)$$


# Pole-Zero Cancellation (cont'd)

Zero cancels the old 2<sup>nd</sup> pole:

(zero)  $\frac{g_{m5}}{(g_{m5}R_C - 1)C_Z} = \frac{g_{m5}}{C_L}$ ; (old 2<sup>nd</sup> pole)

$\chi = \frac{C_Z}{g_{m1,2}R_Z C_I}$  separation with p3(new)

$C_L = g_{m5}R_C C_Z - C_Z$

$R_Z = \frac{C_Z}{\chi g_{m1,2} C_I}$

$\frac{g_{m5}}{\chi g_{m1,2} C_I} C_Z^2 - C_Z - C_L = 0$

(Using a different notation for Cc)

Use eqns (1) & (2) to solve Cz:

Cc derived earlier without Rz (assume same  $\chi$ )

$C_Z = \frac{\chi g_{m1,2} C_I \left( 1 + \sqrt{1 + \frac{4g_{m5} C_L}{\chi g_{m1,2} C_I}} \right)}{2g_{m5}} \approx \sqrt{\frac{\chi g_{m1,2} C_I C_L}{g_{m5}}}$

$\sim C_C = \chi \frac{g_{m1,2}}{g_{m5}} C_L$

$R_Z = \sqrt{\frac{C_L}{\chi g_{m1,2} g_{m5} C_I}}$



# Nulling Resistor (cont'd)

The compensation capacitor (**with R**) is named **C<sub>z</sub>** ;  
that **without R** is named **C<sub>c</sub>** .

If choosing **C<sub>z</sub> < C<sub>c</sub>**, we might be able to achieve **higher GBW**.

$$C_z = \sqrt{\frac{\chi g_{m1,2} C_I C_L}{g_{m5}}} \leq C_c = \chi \frac{g_{m1,2}}{g_{m5}} C_L$$



$$C_I \leq \chi \frac{g_{m1,2}}{g_{m5}} C_L$$

$$GBW = \omega_T = \frac{g_{m1,2}}{C_c}$$



$$GBW = \omega_T = \frac{g_{m1,2}}{C_z} \quad \text{Now (Cz is reduced!)}$$

Or

$$\chi \geq \frac{g_{m5}/C_L}{g_{m1,2}/C_I}$$

$f_z = p_2$

$f_T$  of the 1<sup>st</sup> stage with  
nulling resistor

**Choosing this separation factor will help achieve a higher GBW.**

# *Sizing with compensation for Eliminating the RHP Zero*



**Voltage buffer compensation & current buffer compensation.**

# Closed-loop Stability

- For two-stage opamps, adding the Miller capacitor  $C_c$  results in the **pole-splitting phenomenon** which improves the closed-loop stability significantly.
- However, the Miller capacitor also creates a feed-forward path which leads to a **RHP zero**.
- Such a zero can be relocated by connecting a series **nulling resistor**, or
- Connecting a **common-gate current buffer** (Mahattanakul, 2005), etc.

J. Mahattanakul, "Design procedure for two-stage CMOS operational amplifiers employing **current buffer**," IEEE Trans. CAS-II: Express Briefs, vol. 52, no. 11, Nov. 2005, pp. 766-770.


# Voltage/Current Buffer Compensation

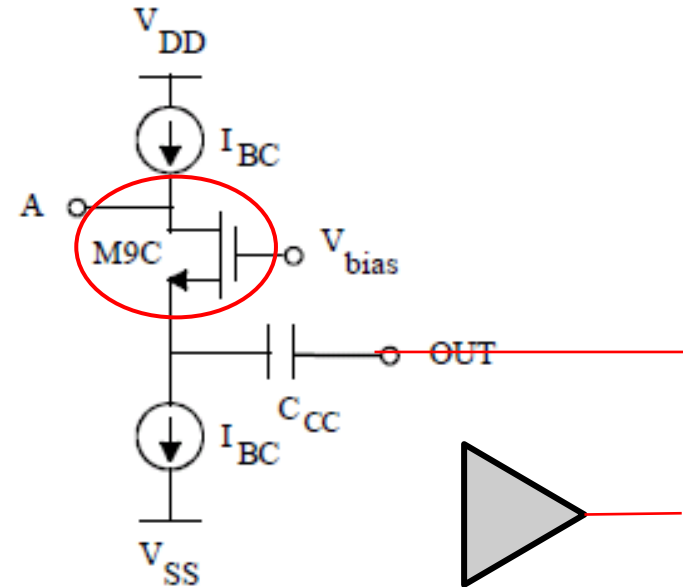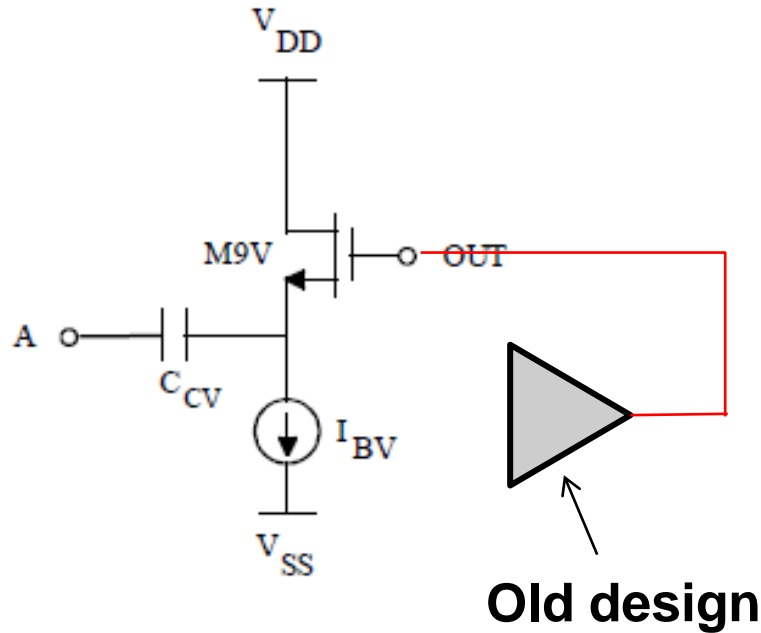

Modification by adding voltage buffer (VB)

Modification by adding current buffer (CB)

# Sizing with Voltage Buffer

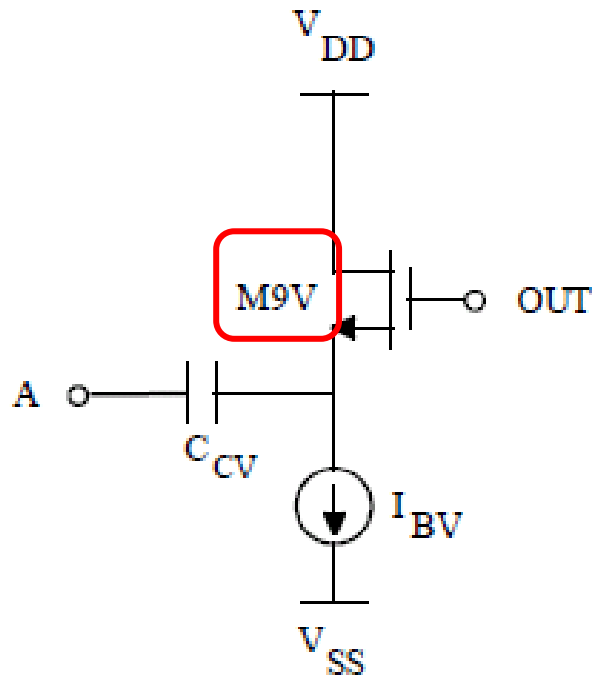

**VB breaks the compensation path into indirect connection, eliminating a possible zero path.**

The buffer transistor **M9** has an output resistance  $1/g_{o,9}$ .

The compensation path introduces a **LHP zero** at

$$f_z = -\frac{g_{o,M9}}{2\pi C_{CV}} \quad \text{cf. the prev lecture}$$

We may let this zero cancel the 2<sup>nd</sup> pole:

$$\frac{g_{m5}}{C_L} = \frac{g_{o,M9}}{C_{CV}}$$

# Cancelling the 2<sup>nd</sup> pole (cont'd)

$$\frac{g_{m5}}{C_L} = \frac{g_{o,M9}}{C_{CV}} \quad (1)$$

This equation has two unknowns:  $g_{o,M9}$  and  $C_{CV}$ .

Second, we derive the **new 2<sup>nd</sup> pole** after inserting the VB:


$$f_2^{new} = \frac{g_{o,M9}}{2\pi C_{eq}}$$

$$C_{eq} = C_I + C_{gs9V} \approx C_I$$

$C_I$  is the 1<sup>st</sup> stage output capacitance

Now new GBW becomes
 
$$f_{GBW}^{new} = \frac{g_{m1,2}}{C_{CV}}$$



New separation factor

$$\chi = \frac{f_2^{new}}{f_{GBW}^{new}} = \frac{g_{o,M9} C_{CV}}{g_{m1,2} C_{eq}} \quad (2)$$

# VB (cont'd)

Use equations (1), (2) to solve:

$$\frac{g_{m5}}{C_L} = \frac{g_{o,M9}}{C_{CV}};$$

$$\chi = \frac{g_{o,M9} C_{CV}}{g_{m1,2} C_{eq}} \approx \frac{g_{o,M9} C_{CV}}{g_{m1,2} C_I}$$

$$g_{o,M9} \approx \sqrt{\chi g_{m5} g_{m1,2} \frac{C_I}{C_L}}$$


$$C_{CV} \approx \sqrt{\chi C_I C_L \frac{g_{m1,2}}{g_{m5}}}$$

$C_{cv}$  approximately equals to  $C_z$  derived before for nulling resistor compensation

*Another paper that presents sizing for  
VB compensation*



# Sizing with VB Compensation

 

Two-stage with voltage buffer (VB) compensation

The stage of Q8-Q9 provides voltage buffer compensation

P. Mandal and V. Sisvanathan, "Macromodeling of the AC characteristics of CMOS op-amps," Proc. IEEE/ACM ICCAD, pp. 334-340, 1993.

# Design Equations

Sizing all transistors into saturation ...

Assume that the **body effect parameters** ( $\lambda_i$ 's) and the bias voltages are independent of the transistor widths.

DC gain:


$$A_0 \approx \frac{g_{m1}g_{m6}}{(g_{ds1} + g_{ds3})(g_{ds6} + g_{ds7})} \approx K \sqrt{\frac{W_1W_6}{W_5W_7}}$$

$K = \mu C_{ox}$

The output resistances of  $g_{ds3}$ ,  $g_{ds6}$  are proportional to the drain currents of M5 & M7, respectively.

# DC Gains (more details)

Approximate dc gain:

 


$$A_0 \approx \left[ \frac{g_{m1}}{(g_{ds1} + g_{ds3})} \right] \left[ \frac{g_{m6}}{(g_{ds6} + g_{ds7})} \right] \approx K \sqrt{\frac{W_1 W_6}{W_5 W_7}}$$


gain of 1<sup>st</sup> stage:

gain of 2<sup>nd</sup> stage:

**Voltage buffer**

 

# Dominant Pole

 

The first pole is

$$p_1 \approx \frac{(g_{ds1} + g_{ds3})(g_{ds6} + g_{ds7})}{C_C g_{m6}} \approx K \frac{W_5}{C_C} \sqrt{\frac{W_7}{W_6}}$$


$$p_1 \approx \frac{(g_{ds1} + g_{ds3})(g_{ds6} + g_{ds7})}{C_C g_{m6}} = \frac{1}{R_I (C_C g_{m6} R_{II})}$$

Miller effect  $C_c$

# Sizing

The  $I_{D,3}$  is half  $I_{D,5}$ ; and the drain currents of  $I_{D,6} = I_{D,7}$  are equal.

It follows that:

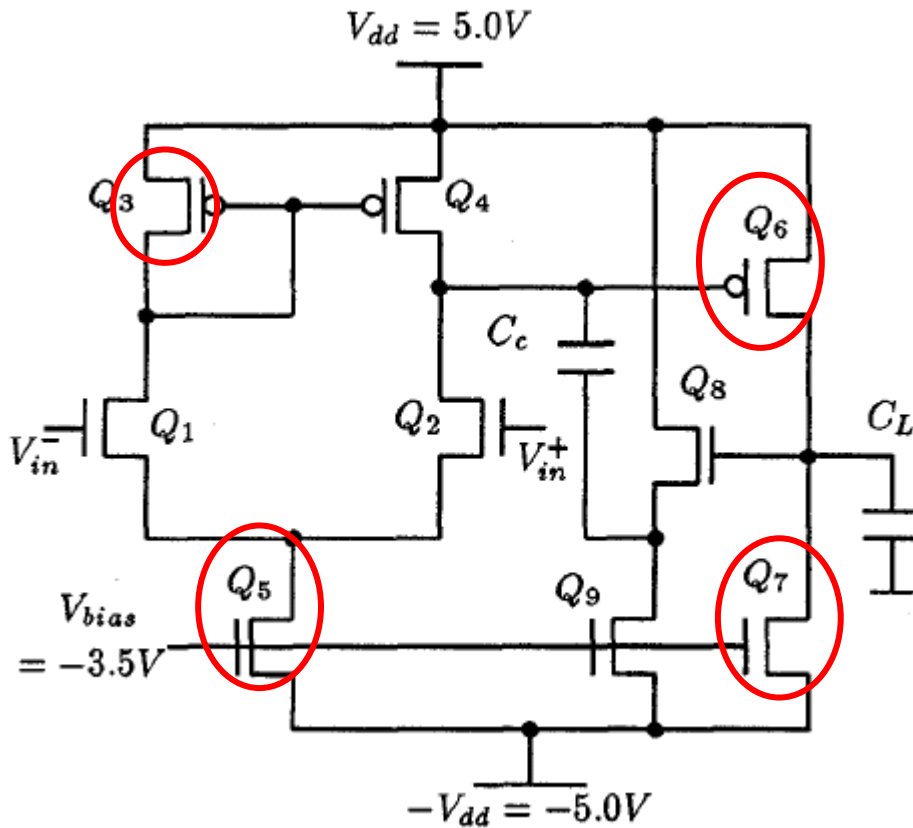


$$\frac{\left(\frac{W}{L}\right)_3 (1 - \lambda_p V_{ds,3})}{\left(\frac{W}{L}\right)_6 (1 - \lambda_p V_{ds,6})} = \frac{\frac{1}{2} \left(\frac{W}{L}\right)_5 (1 + \lambda_n V_{ds,5})}{\left(\frac{W}{L}\right)_7 (1 + \lambda_n V_{ds,7})}$$

Assume:

$$(1 - \lambda_p V_{ds,3}) = (1 + \lambda_n V_{ds,5})$$

$$\lambda_p \approx \lambda_n$$


$$-V_{ds,6} = V_{ds,7}$$

 

$$\frac{W_6}{W_7} = 2 \frac{W_3}{W_5}$$

# *Other mentioning of the literature*

# Sizing for Current Buffer Compensation

 

**Current buffer**

According to (Palmisano and Palumbo, 1997), the optimal GBW is achieved by

$$g_{m9C} = 2g_{m1,2};$$

$$C_{CC} \approx \sqrt{\frac{g_{m1,2}}{g_{m5}} \left( \frac{2K-1}{2+K} + \frac{1}{2} \right)} C_L C_I$$

$$K = \mu C_{ox}$$


Also called **common gate current buffer Miller compensation (CBMC)**

G. Palmisano and G. Palumbo, "A compensation strategy for two-stage CMOS opamps based on current buffer," IEEE Trans. on CAS-I, vol. 44, no. 3, pp. 257-262, March 1997.
 
# Caution on Doublet

The current mirror (**M3-M4**) may introduce a **pole-zero doublet** with  $s_z > 2*s_p$ .

The doublet **can be ignored in the traditional design**, but must be considered **with  $R_z$ ,  $V_B$ , and  $CB$  compensations** due to the **higher GBW**.



\* The issue of doublet is discussed in another lecture.



# Doublet Issue (cont'd)

The **doublet-pole** frequency is approximately (**verify?**) at

$$f_{db} \approx \frac{g_{m3,4}}{2\pi 2C_{gs4}}$$

The new GBW is approximately given by (cf. Palmisano and Palumbo, 1999):

$$f_{GBW}^{new} \approx \frac{2f_2 f_{db}^2}{\chi f_{db} (f_{db} + f_2)}$$

The **new compensation capacitor** can be calculated by:

$$C_{C,new} \approx \frac{f_{GBW} C_C}{f_{GBW}^{new}}$$

G. Palmisano and G. Palumbo, "Analysis and compensation of two-pole amplifiers with a pole-zero doublet," IEEE Trans. on CAS-I, vol. 46, no. 7, pp. 864-868, July 1999.

# *Paper Reading*

---

**The following paper is recommended for reading**

- **J. Mahattanakul, “Design procedure for two-stage CMOS operational amplifiers employing current buffer,” IEEE Trans. CAS-II: Express Briefs, vol. 52, no. 11, Nov. 2005, pp. 766-770.**
- **containing detailed small-signal analysis and sizing info.**

# References

- P. E. Allen and D. R. Holberg, CMOS Analog Circuit Design, 2<sup>nd</sup> ed. Oxford University Press, Oxford, 2002.
- B. K. Ahuja, “An improved frequency compensation technique for CMOS operational amplifiers,” IEEE J. Solid-State Circuits, vol. SC-18, no. 3, pp. 629–633, Jun. 1983. (original proposal of the current buffer technique, but lacks detailed analysis)
- G. Palmisano, G. Palumbo, and S. Pennisi, “Design procedure for two-stage CMOS transconductance operational amplifiers: a tutorial,” Analog Integrated Circuits and Signal Processing, vol. 27, pp. 179-189, 2001. (introduced in this lecture)
- G. Palmisano and G. Palumbo, “A novel representation for two-pole feedback amplifiers,” IEEE Trans. on Education, vol. 41, no. 3, Aug. 1998, pp. 216-218.
- J. Huijsing, R. Hogervorst, and K. de Langen, “Low-power low-voltage VLSI operational amplifier cells,” IEEE Trans. on Circuits and Systems – II, vol. 42, pp. 841-852, Nov. 1995.
- G. Palmisano, G. Palumbo, and R. Salerno, “CMOS output stages for low voltage power supply,” IEEE Trans. on CAS – II, vol. 47, no. 2, pp. 96-104, Feb. 2000.

# *Appendix*