



A PSpice Tutorial

Guoyong Shi, PhD

shiguoyong@ic.sjtu.edu.cn

School of Microelectronics


Shanghai Jiao Tong University

Fall 2009

History

- SPICE – **S**imulation **P**rogram with **I**ntegrated **C**ircuit **E**mphasis
- Developed by University of California at Berkeley starting mid-1970s
- In 1984 MicroSim Corporation (now Cadence) made SPICE available for PC under the name PSpice.


OrCAD PSpice

 

Free Download

- PSpice Demo version can be downloaded (free) from www.orcad.com
- My OrCAD_Demo version was installed in C:\Program Files\OrCAD_Demo\
- For model library, add the line in netlist:
`.lib "nom.lib"`

Example – DC Analysis

 

The first line is always a comment.

*DC1.CIR – SERIES CIRCUIT

VSOURCE 1 0 5

R1 1 2 1K

R2 2 3 2K

R3 3 0 3K

start

end inc (>0)

.DC VSOURCE 6 6 1


.PRINT DC V(2,3) V(2) I(R2)

.END

Example


```
*DC2.CIR – SERIES CIRCUIT  
  
VSOURCE 1 0 5  
  
R1 1 2 1K  
  
R2 2 3 2K  
  
R3 3 0 3K  
  
.DC VSOURCE 5 10 0.5  
  
* DC analysis from 5 to 10 volts, step 0.5 volts.  
  
.PRINT DC V(2,3) V(2) I(R2)  
  
.PROBE  
  
* Use graphics – a comment line  
  
.END
```

Example

 

```
*DC4.CIR
V1 1 0 5
V2 6 7 8
V3 4 5 10
R1 1 2 100
R2 2 7 200
R3 2 3 300
R4 3 6 400
R5 3 4 500
R6 5 6 600
R7 7 0 700
.DC V1 5 5 1
.PRINT DC I(R4)
.END
```


Example – Transient Analysis

 

*TR1.CIR – Resistor Capacitor
V1 1 0 PULSE(0 5 0 1N 1N 5M 10M)
R1 1 2 1K
C1 2 0 1U
.TRAN 1M 10M time step duration
.PROBE
.PRINT TRAN V(2) V(1,2) I(R1)
.END

PULSE([low] [high] [delay] [rise] [fall] [duty] [period])

Switch Model

 

Voltage Controlled
Switch (V1 high – ON,
V1 low – OFF)

Controlled by


*SW.CIR – Resistor Inductor
.MODEL V_SWITCH VSWITCH
V1 1 0 PULSE(0 5 0 1N 1N 5M 10M)
R1 2 3 1K
R2 2 0 1K
L1 3 0 1
S1 2 1 1 0 V_SWITCH
.TRAN 0.1M 10M
.PROBE
.END

Model name


Model type

Simulation Result

SW.CIR

 

Example – AC Analysis

 


```
*AC1.CIR – AC SOURCE  
V1 1 0 SIN(0 5 1000)  
R1 1 2 1K  
C1 2 0 .159U  
.TRAN .1M 5M  
.PRINT TRAN V(1) V(1,2) V(2)  
.PROBE  
.END
```

SIN([DC_offset] [amplitude] [freq] [delay] [damping_factor] [phase])

Simulation Result

AC01.CIR

 

Note the 45 degree phase shift.

Output syntax

.TRAN 0.1M 5M 4M 0.01M


**No print until 4M. Refined time-step 0.01M.*

.PRINT DC V(4) V(5,6) I(Vsource)

**The current output variable has the form I(Vname).*

**For PSPICE, it can be I(Rname).*

Example – Frequency Sweep

 


Decade scale (log)

.AC DEC [pts] [low_f] [hi_f]

```
*AC5.CIR – RESONANT
V1 1 0 AC 5
C1 1 2 0.253U
L1 2 3 1M
RCOIL 3 4 12
RLOAD 4 0 200
.AC DEC 100 10 100MEG
.PROBE
.END
```

Simulation Result


AC5.CIR

 

V4

I(LOAD)

High-Pass Filter

 

*AC8.CIR - Multi-stage high pass circuit

Vs 1 0 AC 10

C1 1 2 0.159U

C2 2 3 0.159U

C3 3 4 0.159U

R1 2 0 1K

R2 3 0 1K

R3 4 0 1K


.AC DEC 100 10 10MEG

.PROBE

.END

Result


AC8.CIR

 

Electronic Circuitry


- The writers of PSpice have created libraries of diodes, op amps, and transistors.
- In the evaluation version of PSpice, there is only one library. All diodes, op amps, and transistors have been modeled in EVAL.LIB.

Diode

 


```
*DIODE00.CIR -- 1N4148 DIODE TEST  
.LIB "NOM.LIB"  
V1 1 0 5  
*D1 1 0 D1N4148  
D1 1 0 MBD101  
.DC V1 0 1 0.01  
.PROBE  
.END
```

MBD101

 

Diode

 

*DIODE01.CIR -- Half wave
rectifier

.lib "nom.lib"

V1 1 0 SIN(0 12.6 1000)

D1 1 2 **D1N4148**

R1 2 0 1K


.TRAN 0.1M 10M 5M 0.01M

.PROBE


.END

Simulation

DIODE01.CIR

 

Bridge Rectifier

 

Rectifier Netlist


*RECTIFIER.CIR -- Full wave rectifier with filter

```
.lib "nom.lib"
V1 1 0 SIN(0 170 60)
Rprimary 1 2 42
Lprimary 2 0 2
Rsecondary 3 4 1
Lsecondary 3 5 0.0221
K1 Lprimary Lsecondary 0.999
```


```
D1 4 6 D1N4148
D2 0 4 D1N4148
D3 0 5 D1N4148
D4 5 6 D1N4148
C1 6 0 1000U
RLOAD 6 0 1K
.TRAN 0.016 0.32 0 0.60M
.PROBE
.END
```

Simulation Result

RECTIFIER.CIR

 


A Zener Diode Added

 


Voltage Regulation

 With a Zener diode, $V(7)$ is better regulated.




Transistor Circuit

 

* source ONE_TRANSISTOR

R_R1 1 2 10k
R_R2 3 5 1k
R_R3 0 4 100
V_V2 5 0 5Vdc
Q_Q1 3 2 4 Q2N2222
V_V3 1 0
+SIN 0.6 0.05 1000 0 0 0

Spice Netlist

 

BJT Noise Test

```
vcc 4 0 50  
vin 1 0 ac  
ccouple 1 2 1  
ibias 0 2 100uA  
rload 4 3 1k  
q1 3 2 0 0 test
```

```
.model test npn kf=1e-20 af=1 bf=100 rb=10  
.noise v(3) vin dec 10 10 100k 1  
.end
```

Behavioral Model

VOLTAGE MULTIPLIER

```
V1 1 0 PWL(0 0 1MS 5V 3MS -5V 5MS 5V 6MS 0)
```

```
.PARAM K = 0.4
```

```
V2 2 0 SIN(0 5 250 0 0 0)
```

*MULTIPLIER MODEL

```
Em 3 0 VALUE = {K*V(1,0)*V(2,0)}
```

```
R0 3 0 100
```

```
.TRAN 0.02MS 6MS
```

```
.PROBE
```

```
.END
```

Table Extension

DIODE CIRCUIT

V1 1 0 DC 15V

R1 1 2 5K

R2 2 0 5K

R3 2 3 10K

R4 3 0 10K

GDIODE 3 4 TABLE {V(3,4)} = (0 0) (0.1 0.13E-11)

+ (0.2 1.8E-11) (0.3 24.1E-11) (0.4 0.31E-8) (0.5 4.31E-8)

+ (0.6 58.7E-8) (0.7 7.8E-6)

R5 4 0 10K

.DC V1 15 15 1

.PRINT DC I(R5)

.END

Freq Extension

FILTER CHARACTERISTIC

VIN 1 0 AC 1 0

R1 1 0 1K

EFILTER 2 0 FREQ {V(1,0)} = (1.0K, -14, 107) (1.9K, -9.6, 90) (2.5K, -5.9, 72)

+ (4.0K, -3.3, 55) (6.3K, -1.6, 39) (10K, -0.7, 26) (15.8K, -0.3, 17)

+ (25K, -0.1, 11) (40K, -0.05, 7) (63K, -0.02, 4) (100K, -0.008, 3)

R2 2 0 1K

.AC DEC 5 1000 1.0E5

.PROBE V(2) V(1)

.END

(FREQ, MAG_DB, PHASE)

Acknowledgement

- The examples in this tutorial are mostly taken from the textbook:

***Robert Lamey, The Illustrated Guide to Pspice,
Delmar Publishers Inc., 1995.***